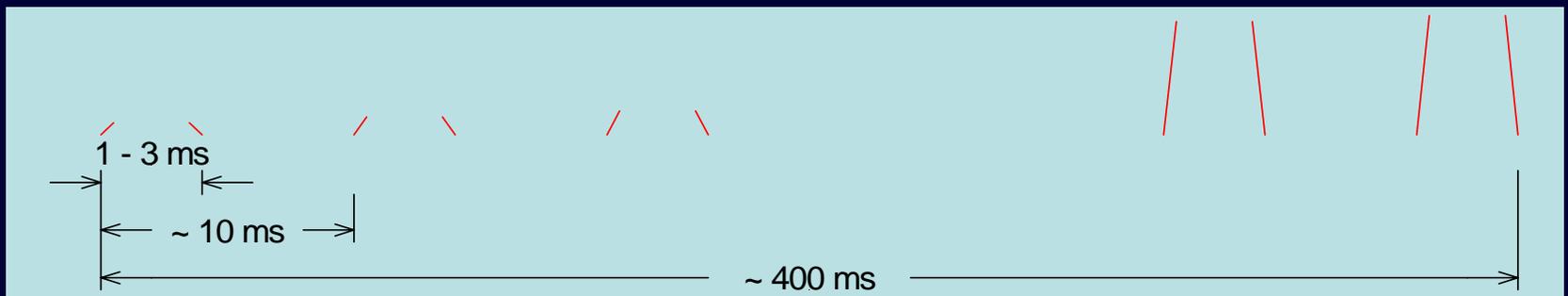
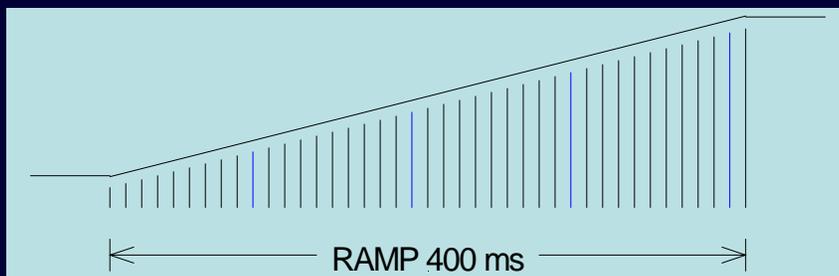

Polarized Proton Beam Weak Resonance Correction by Pulsed Quads

Arlene Zhang, Jon Sandberg

July 16, 2008


Main Specifications



- 41 pairs of +/- tune jumps during 400 ms ramp
- AGS cycle 2.5 s to 4 s
- 4 quads in AGS D5, I5, J5, L5
- 240 A to 2400 A pulsed current

Pulse Waveform Specifications

Option 1 – Trapezoidal

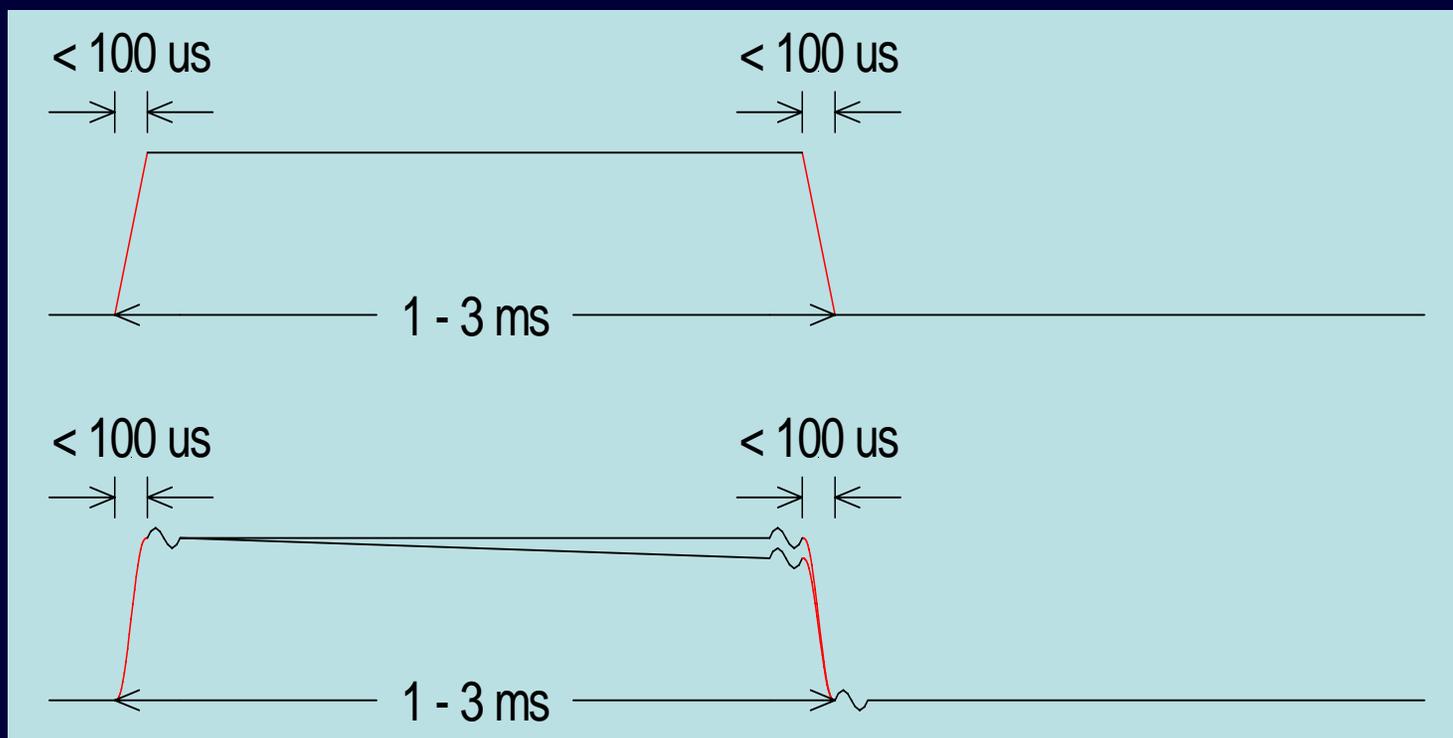

RMS Current

- 240A to 2400A, 54A step
- 100 us rise or fall time
- 1ms flat top or decay time
- 400 ms AGS ramp time
 - RMS current (ramp) = 148.83 A
- Per AGS cycle 2.5s
 - RMS Current (AGS cycle) = 23.813 A
- Per AGS cycle 4.0s
 - RMS Current (AGS cycle) = 14.883 A

RMS Current

Pulse Length	1 ms	2 ms	3 ms
I_rms (Ramp)	148.3 A	284.1 A	419.4 A
I_rms (2.5s AGS cycle)	23.8 A	45.5 A	67.1 A
I_rms (4.0s AGS cycle)	14.9 A	28.4 A	41.9 A

Trapezoidal Pulse: Adjustable flat top

- ? the longer the flat top, the larger the capacitor bank, or the larger the flat top drop.
- ? Symmetric ???


Bipolar Triangle Pulse: Adjustable quiet zone (or adjustable decay)

- ✓ Symmetric


Key Issues

- Cable Inductance
- Pulse Symmetry
- Pulse Overshoot
- Pulse Undershoot
- Pulse Flat-top
- Circuit Resistance
- System Cooling

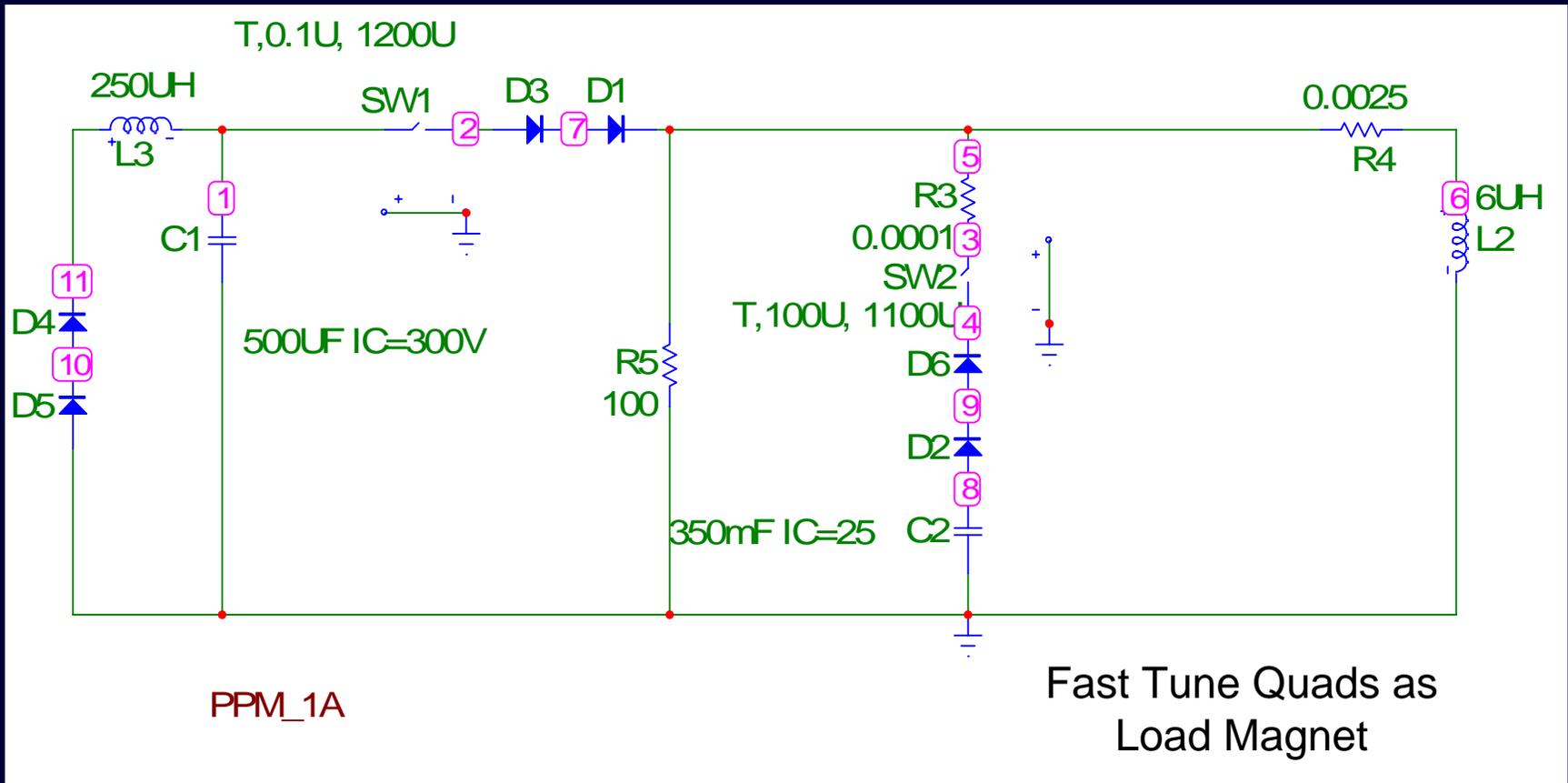
Woody's Suggested Circuit (inside tunnel without cable option)



Simulation

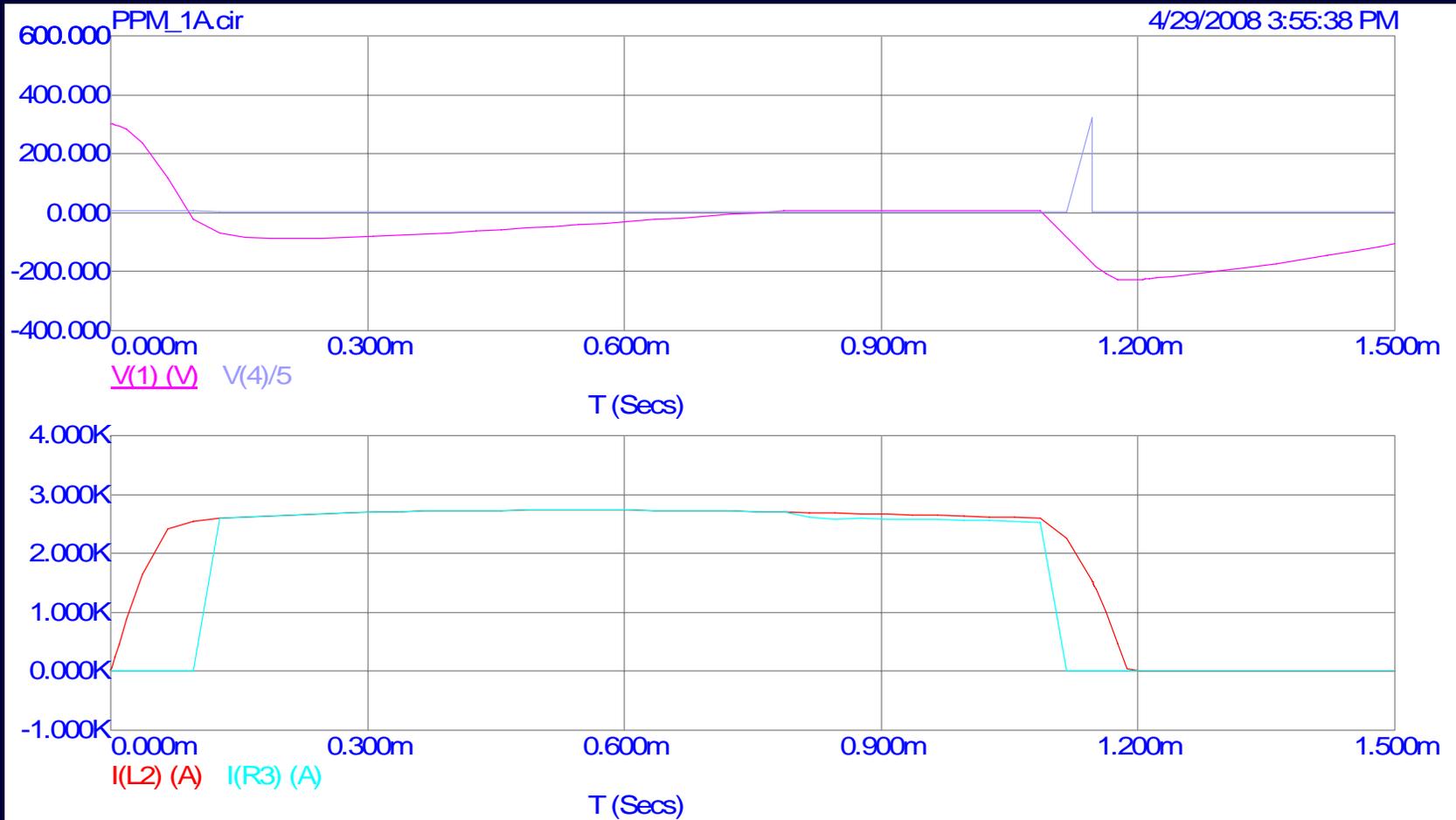


Test Circuit

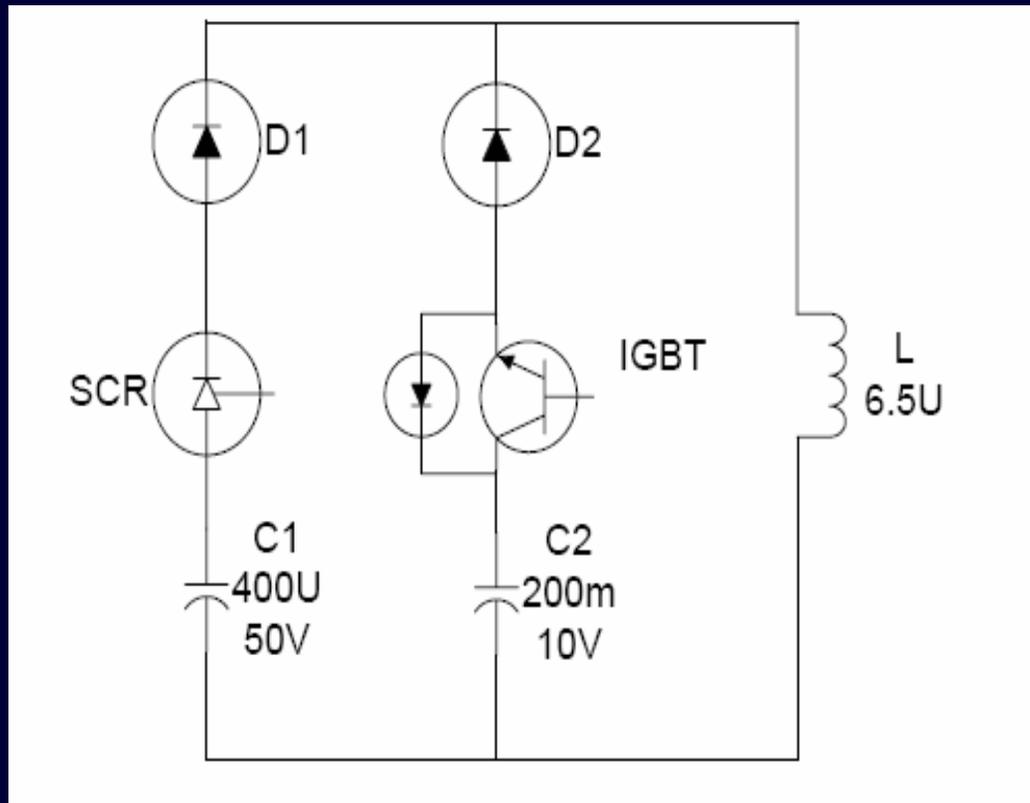


Yugang's test setup

Test Performance

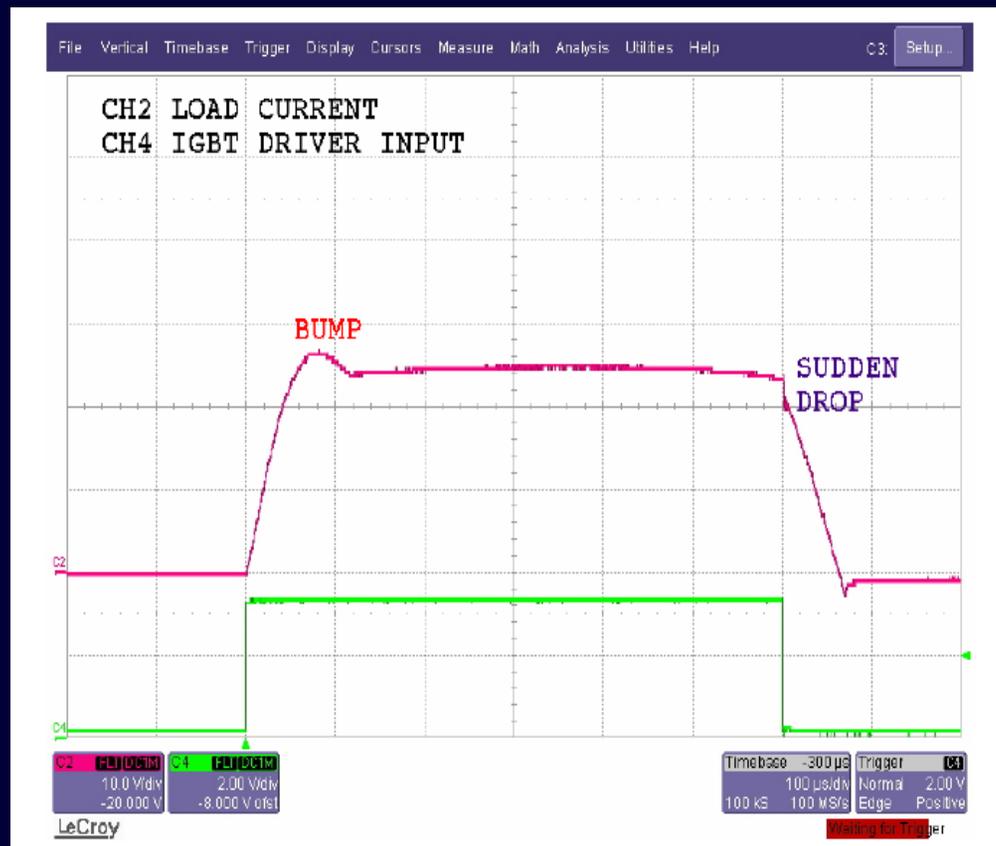


Provided by Yugang Tan

Test Performance

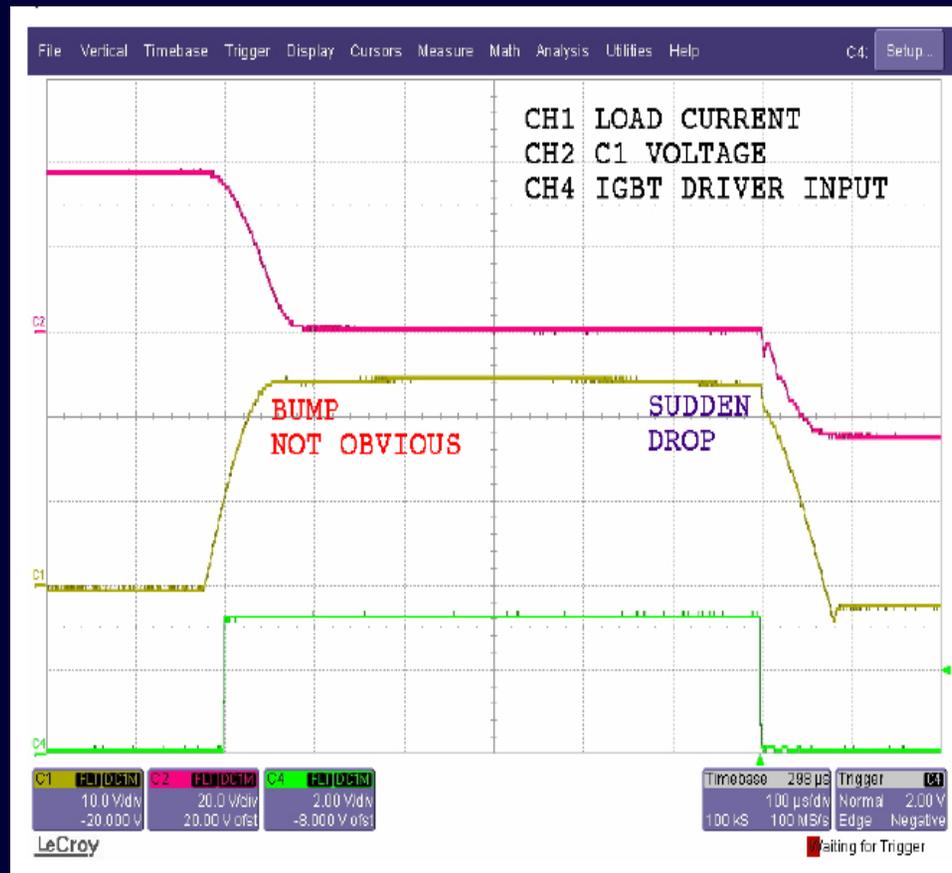


Provided by Yugang Tan

8Q32 with Quadruplex Cable

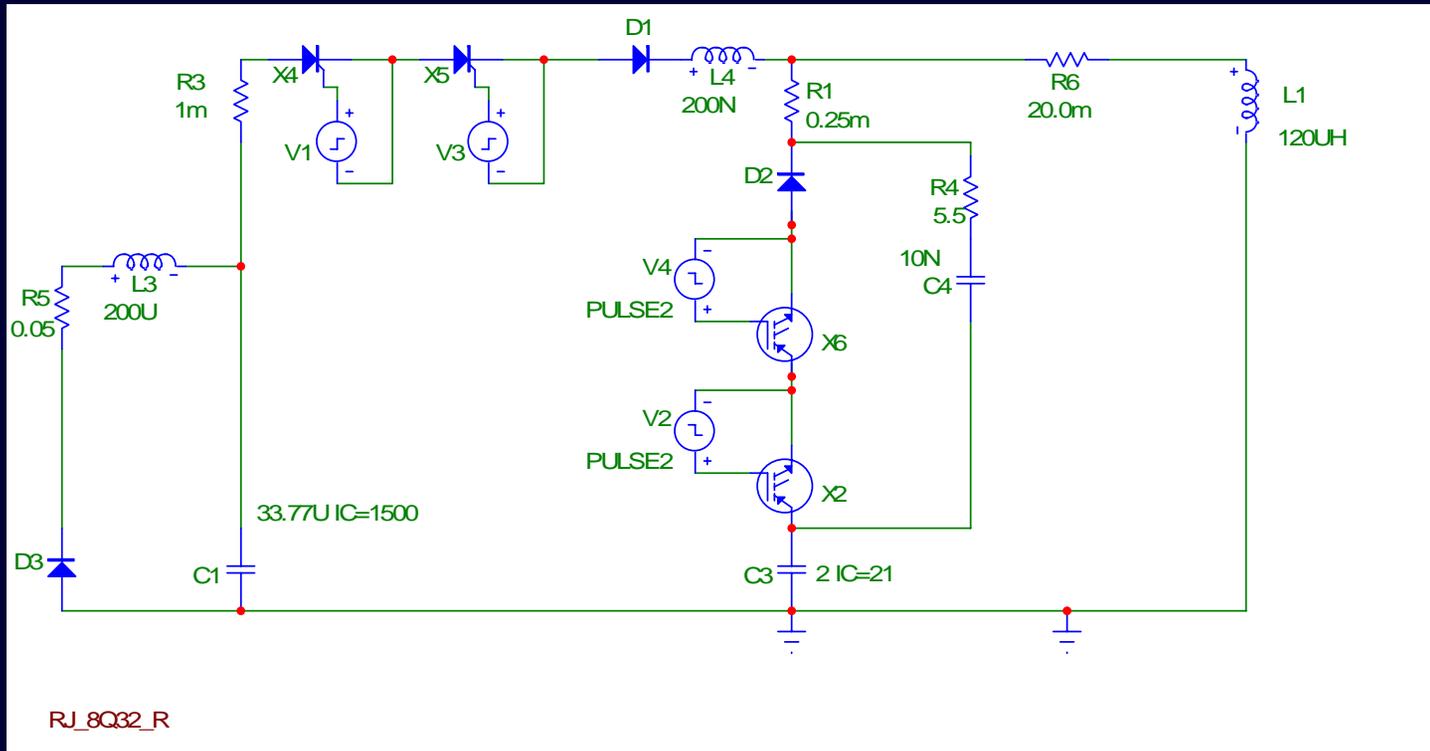

Estimation of cable & load inductance of 120 uH is by Jianlin Mi

Simulation

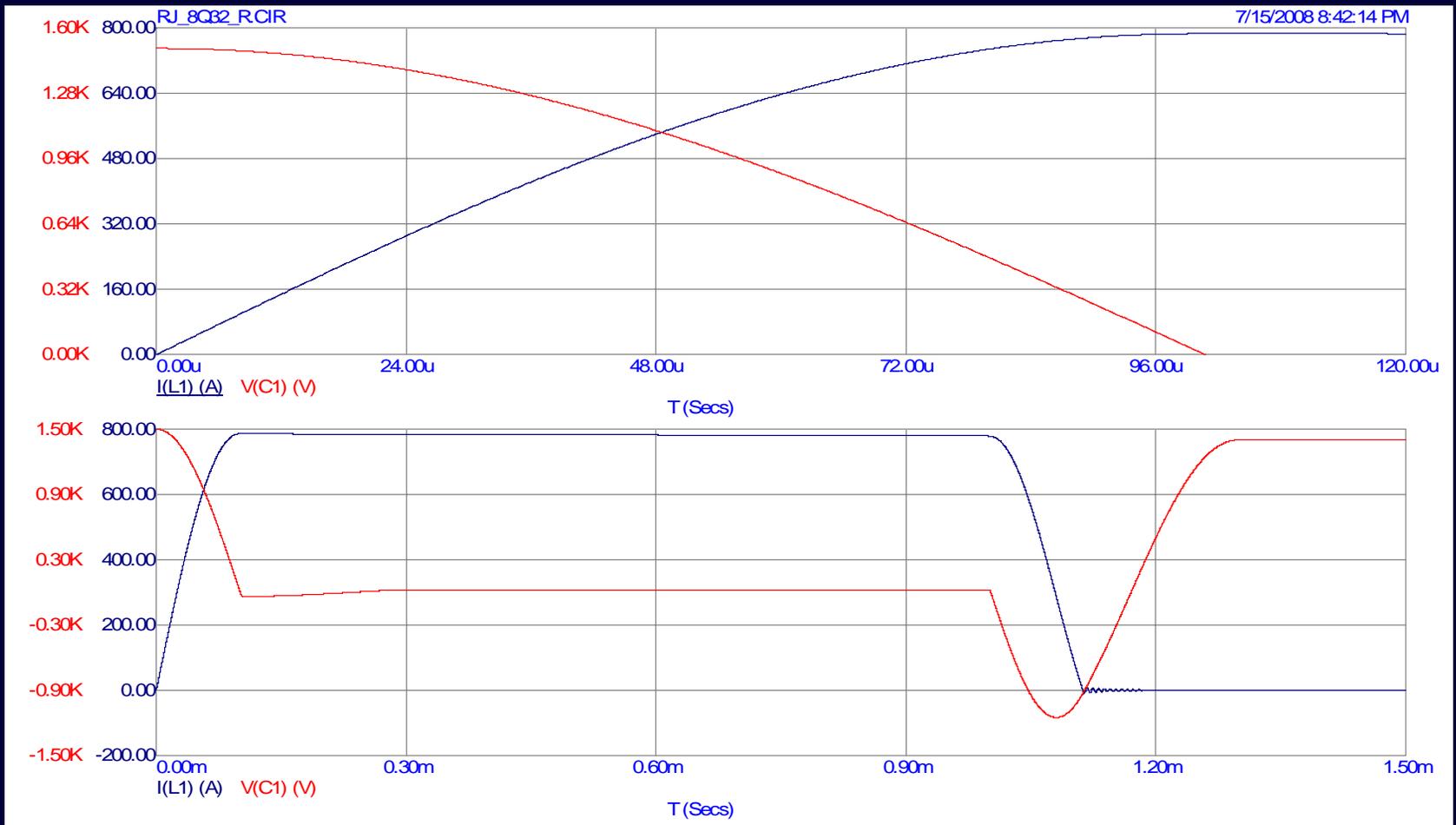


Concerns


- High voltage 1500V
 - Voltage is higher than existing fast bump capacitor rating
- High energy storage
- Large cable inductance
- Inefficiency
- Component Selection

Proposed Schematic

(Fast Tune Quads with Coaxial Cable)

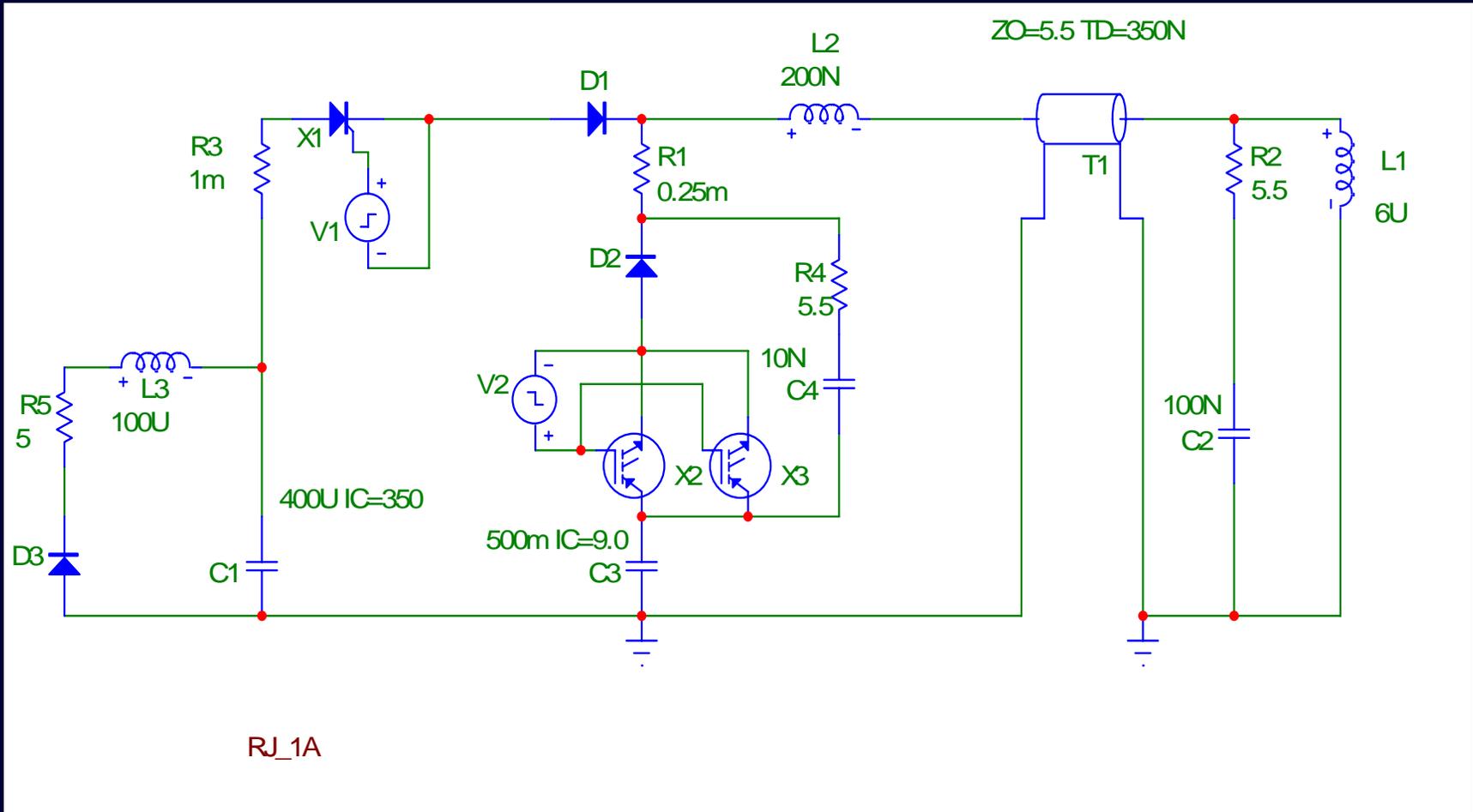


Simulation

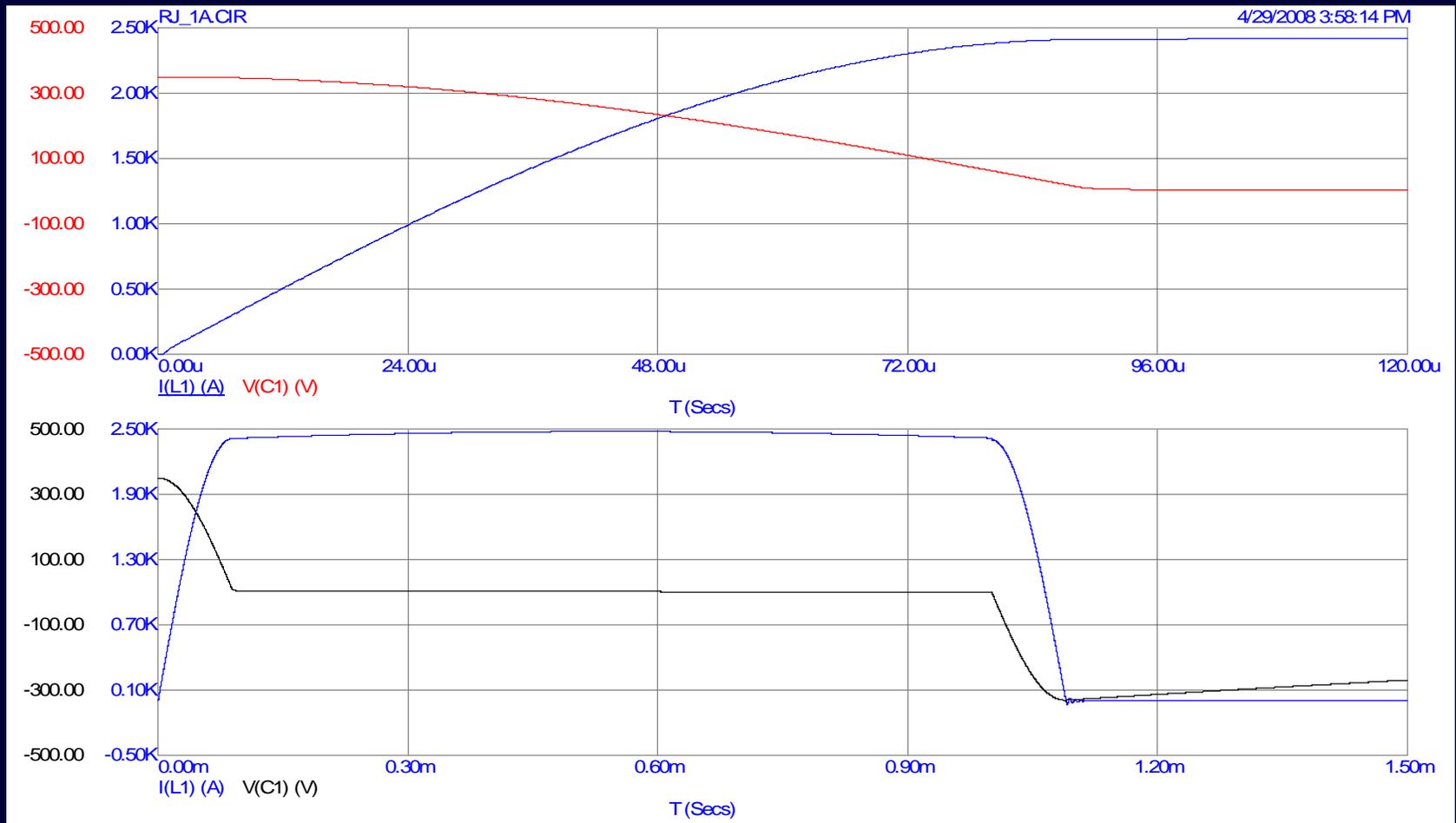


Proposed Test Schematic

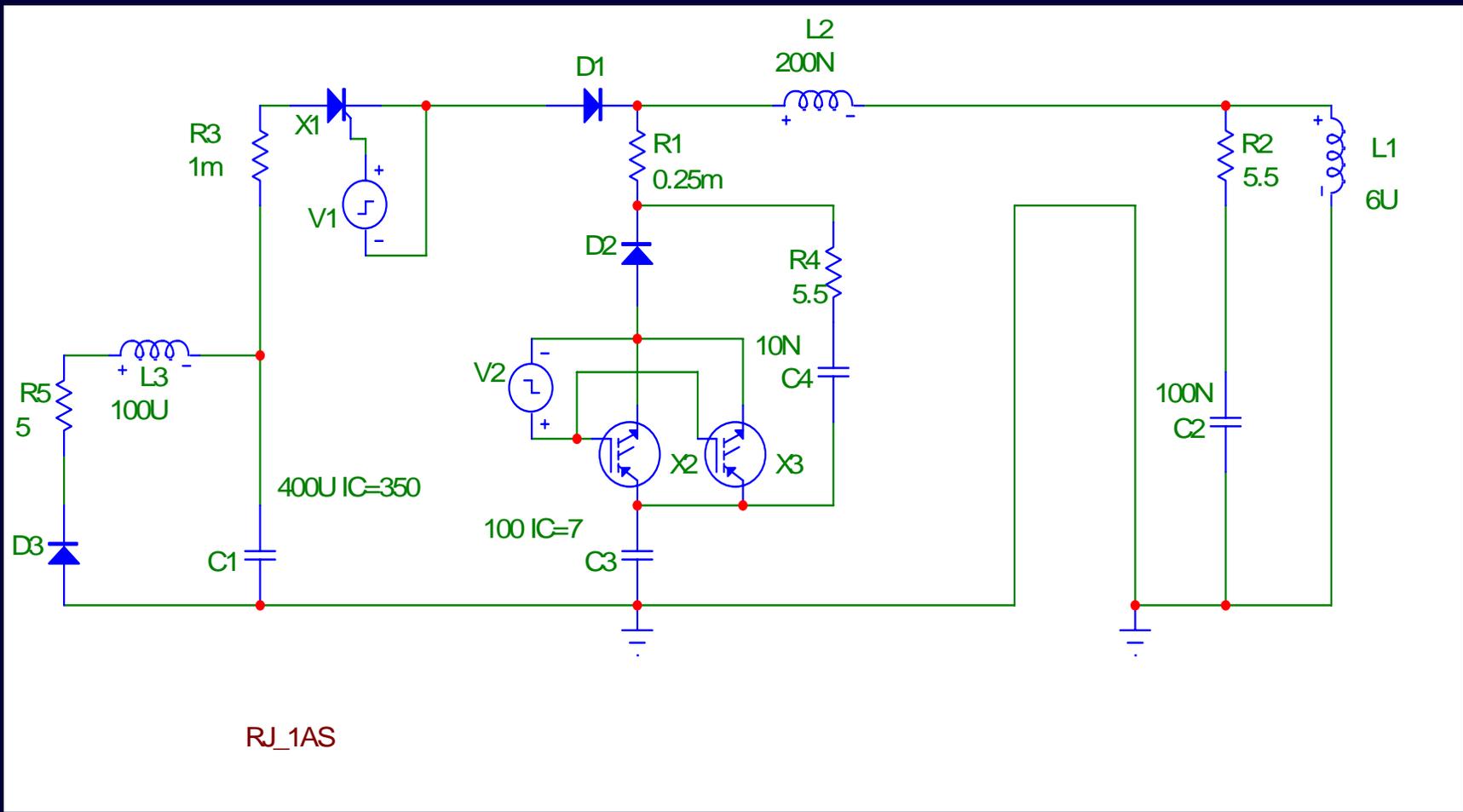
(Fast Tune Quads inside tunnel directly connected)




Simulation

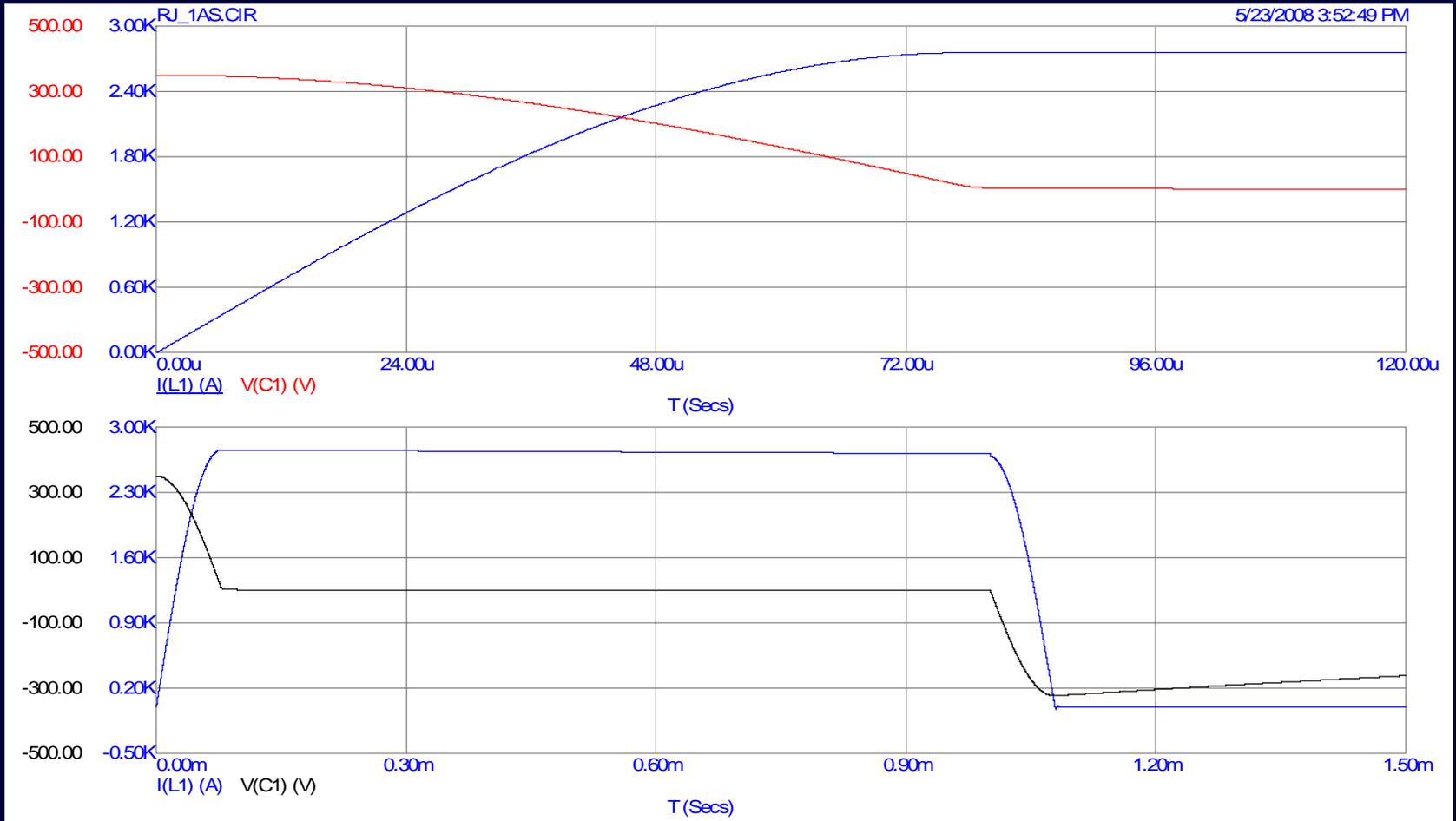

Resistance Effect

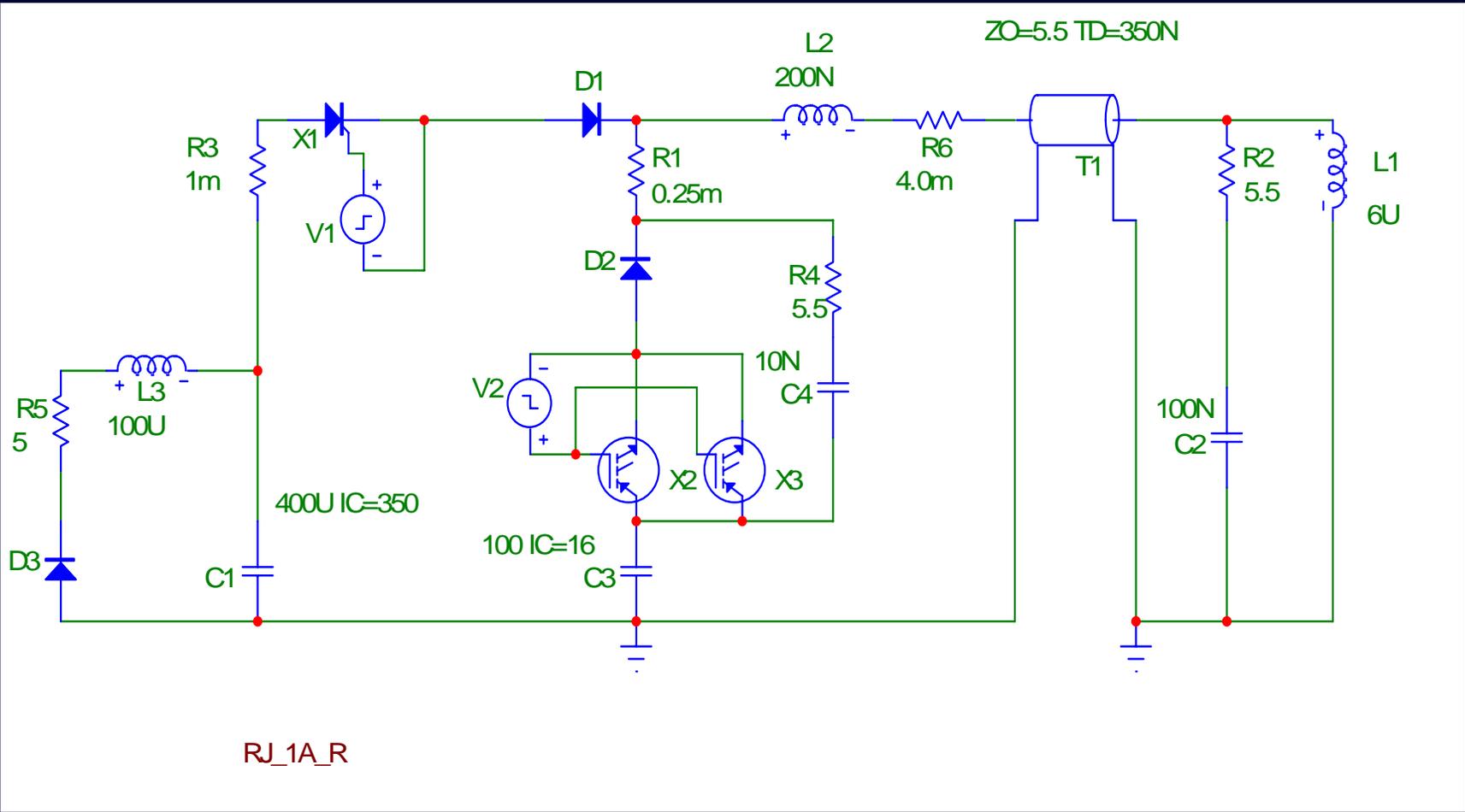


Simulation

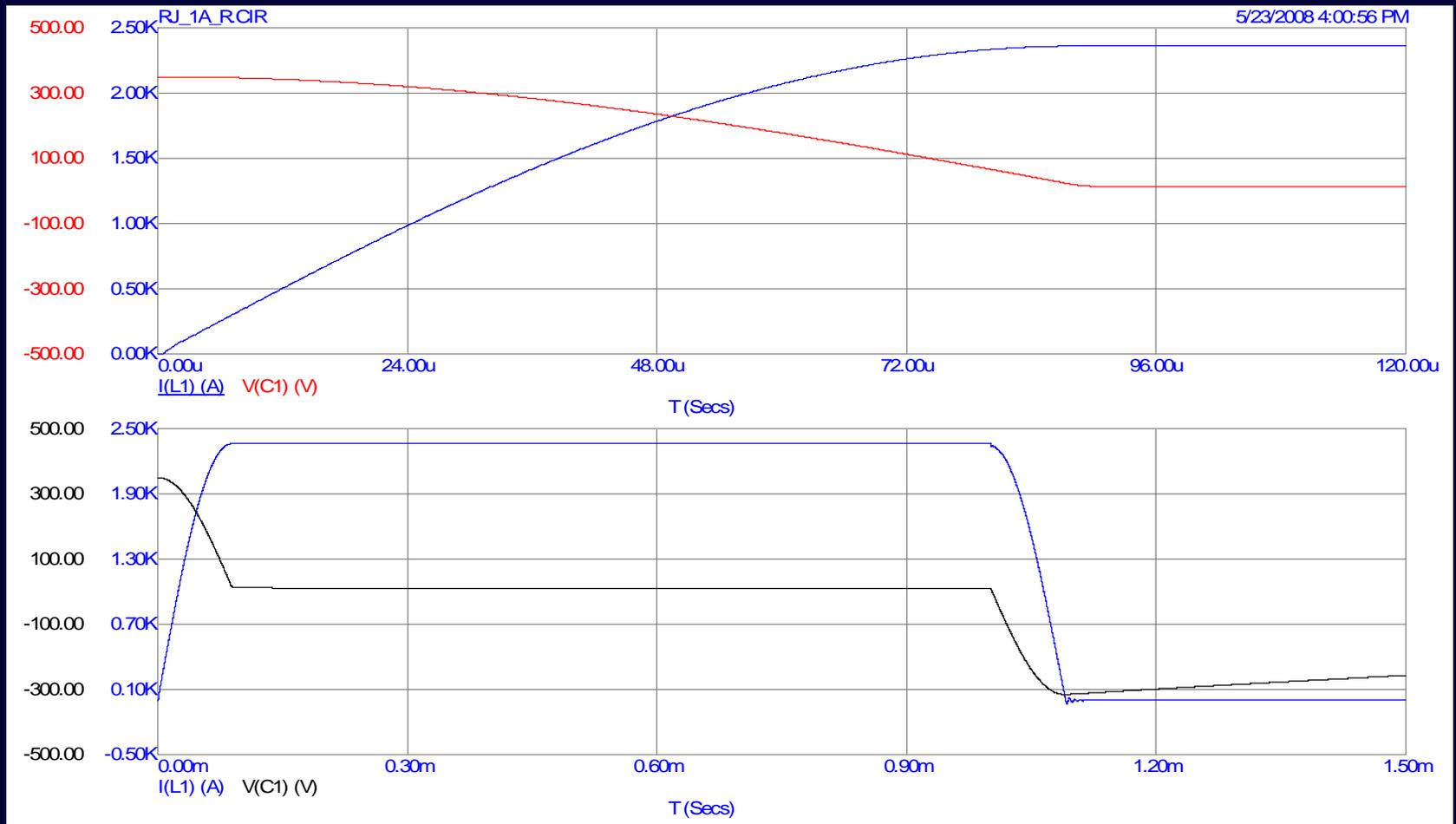


Proposed Schematic


8Q32 with 3 Turn Coil and Coaxial Cable

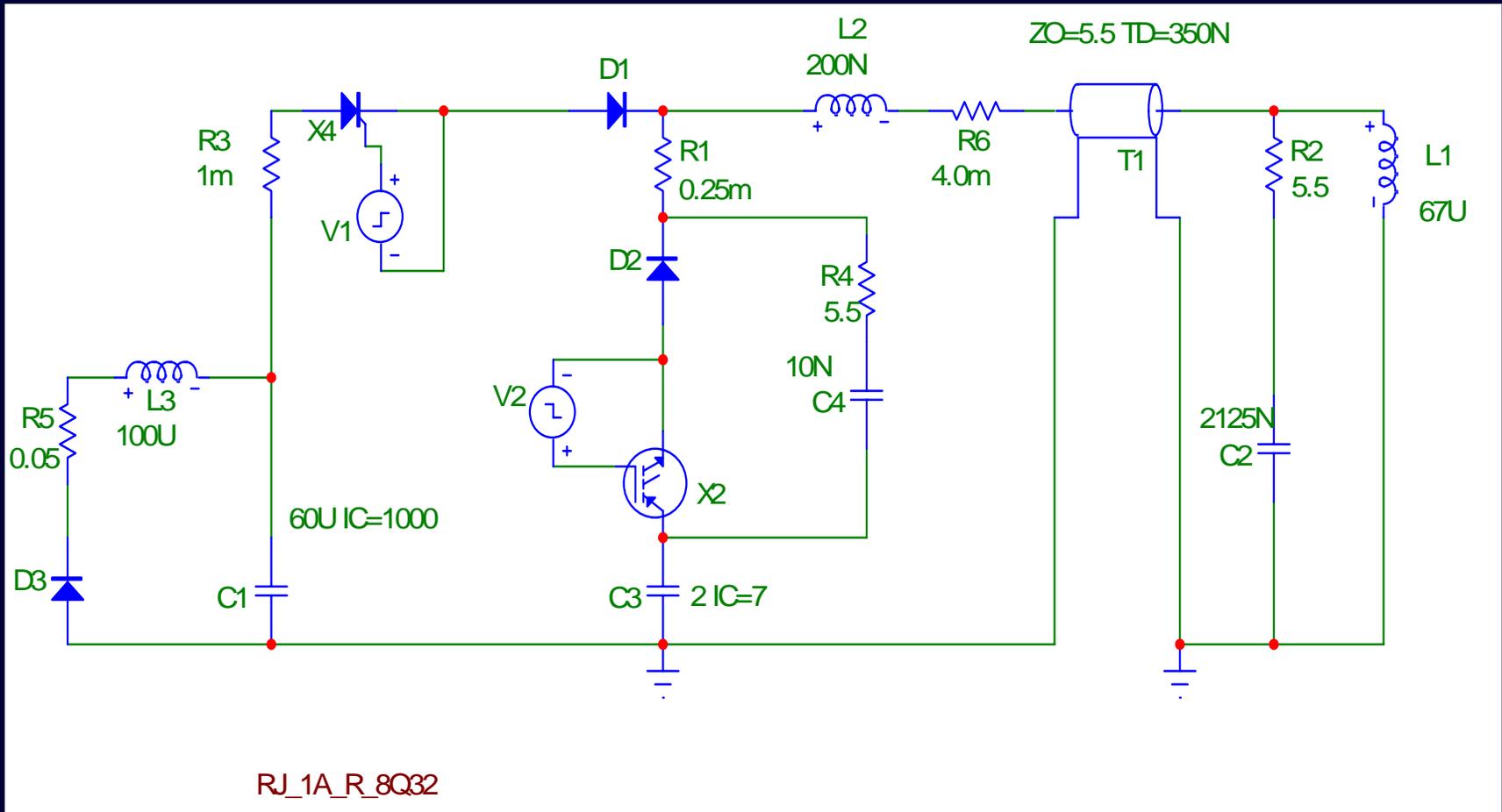


Simulation

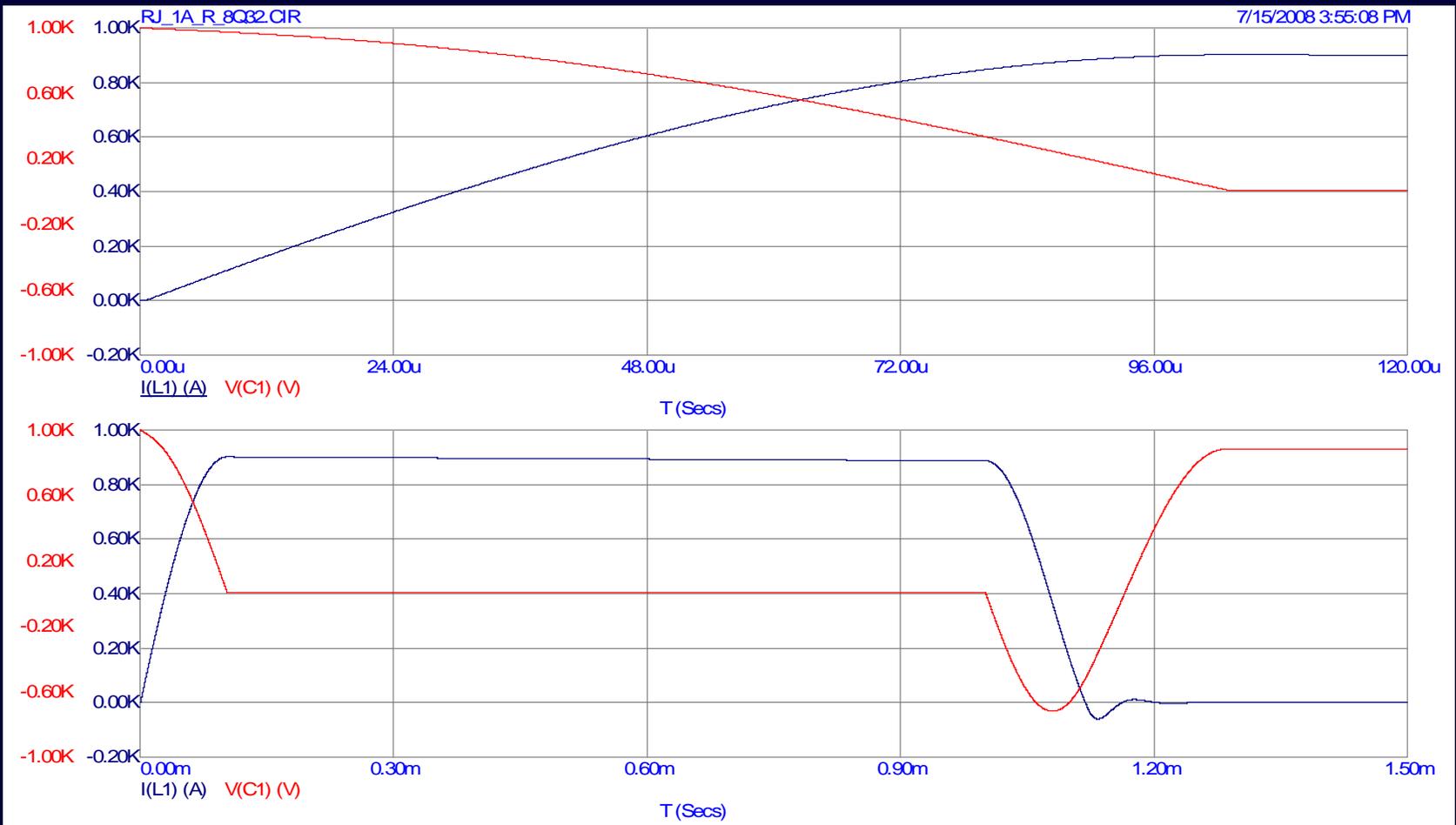

Simulation

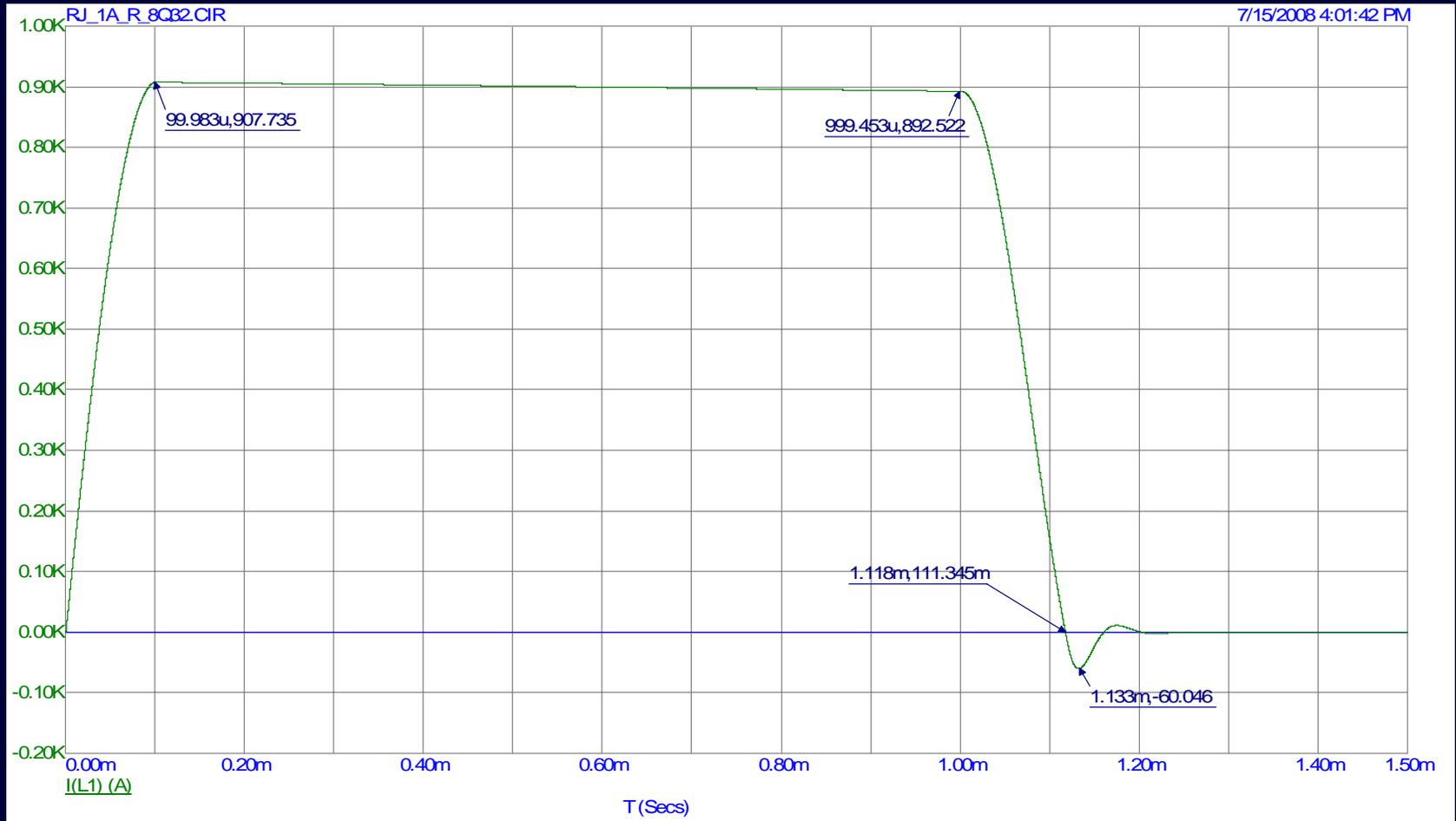


Simulation

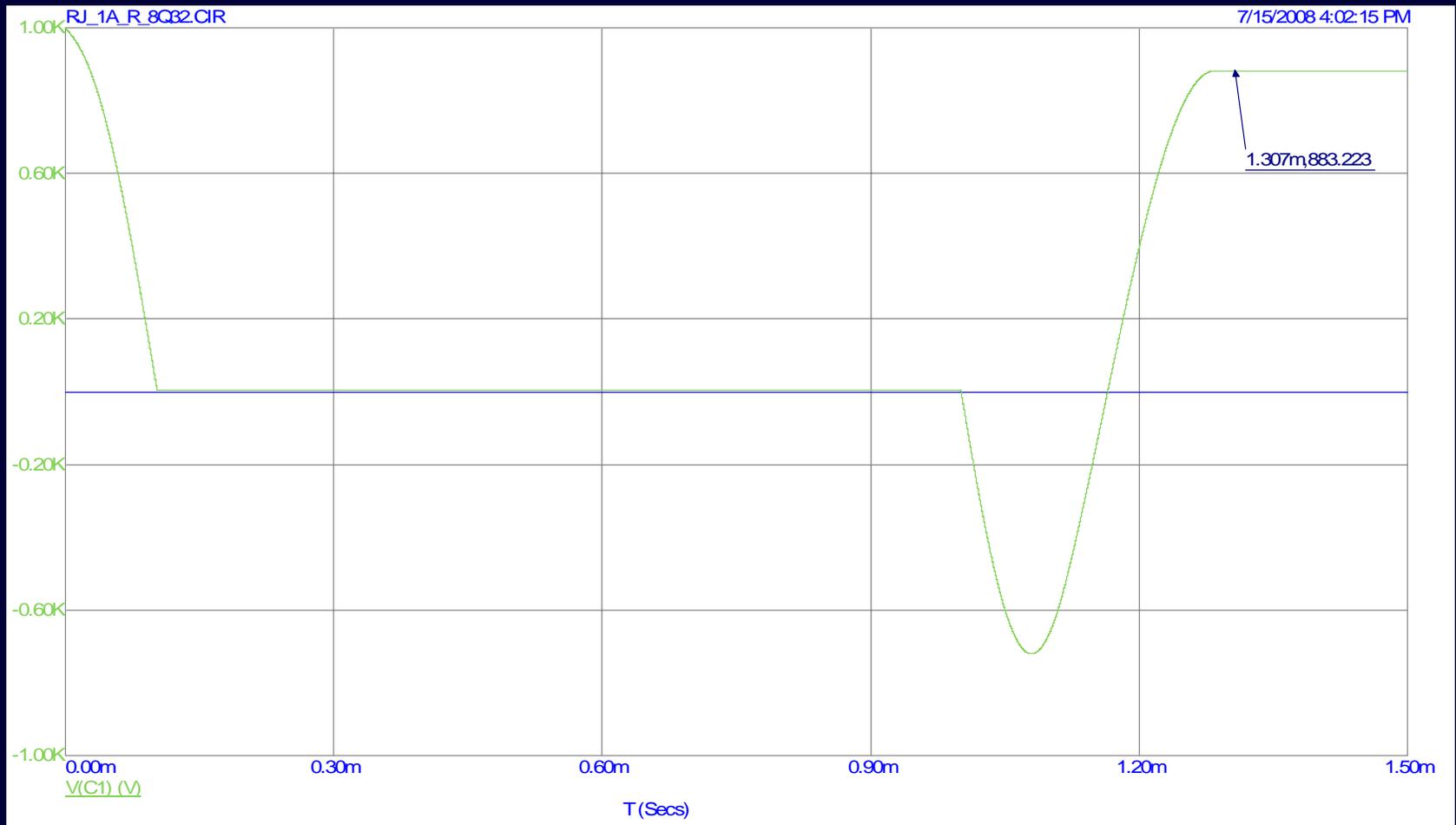


Proposed Schematic

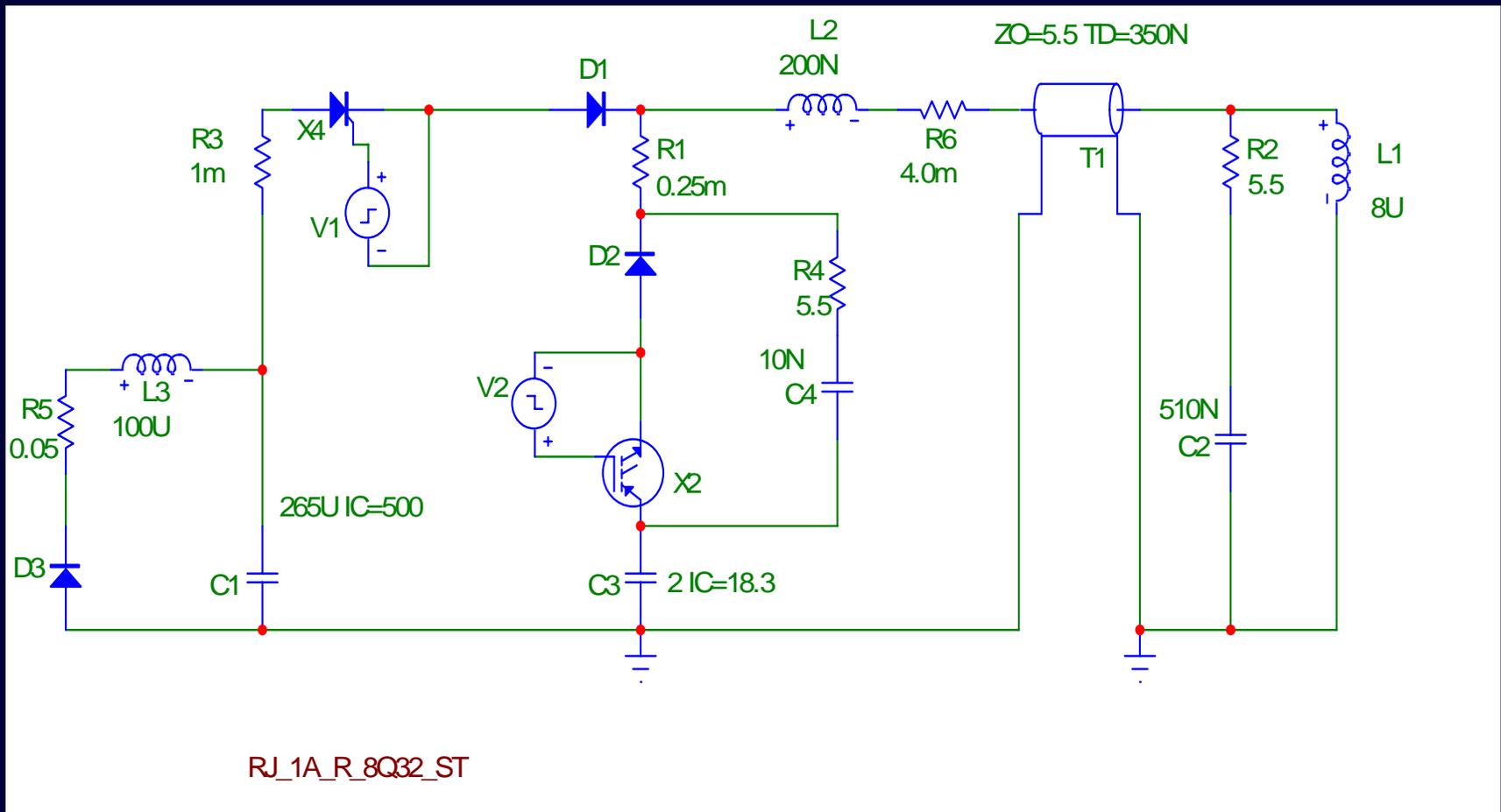
8Q32 with Single Turn Coil and Coaxial Cable




Simulation

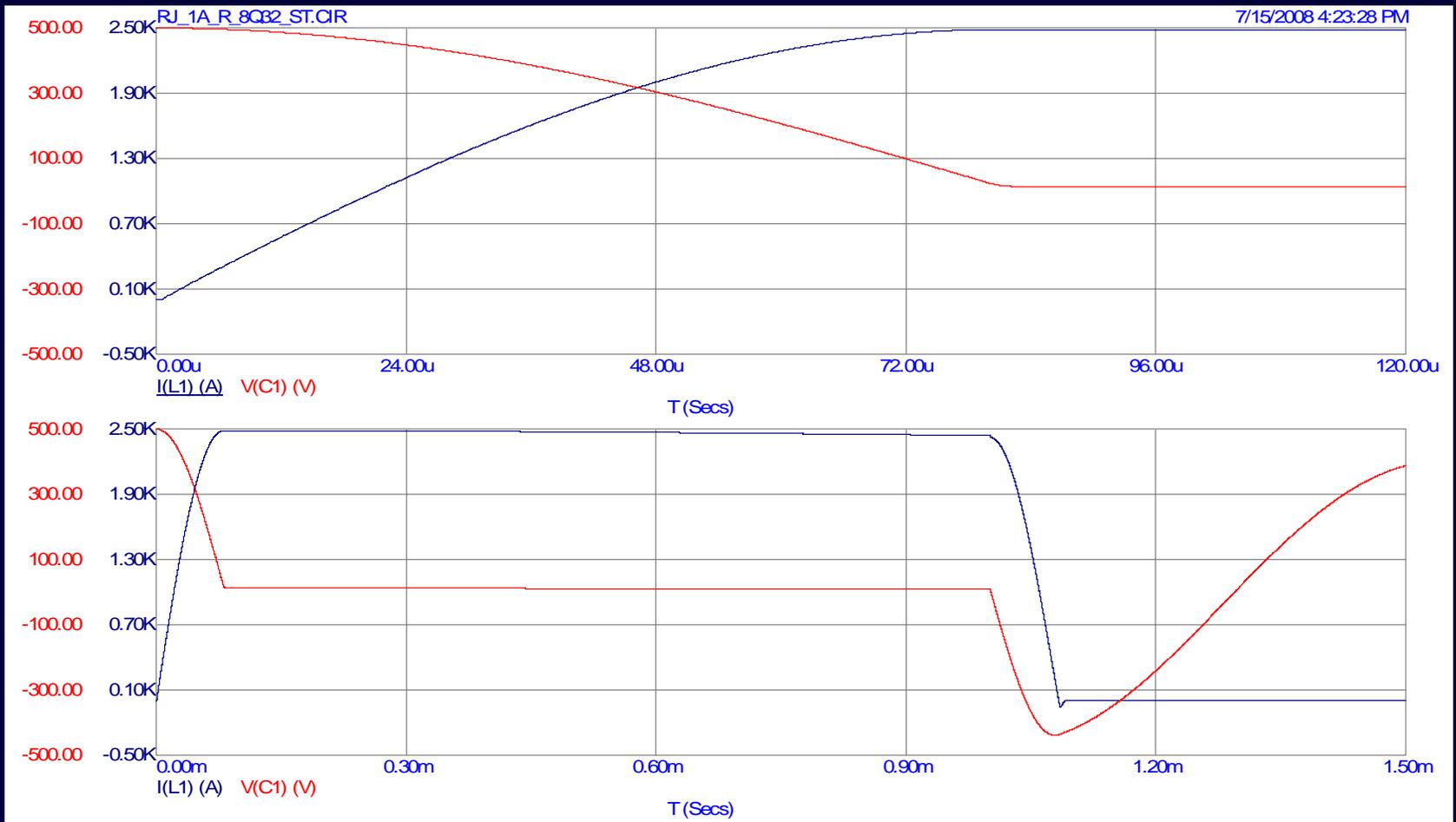


Simulation

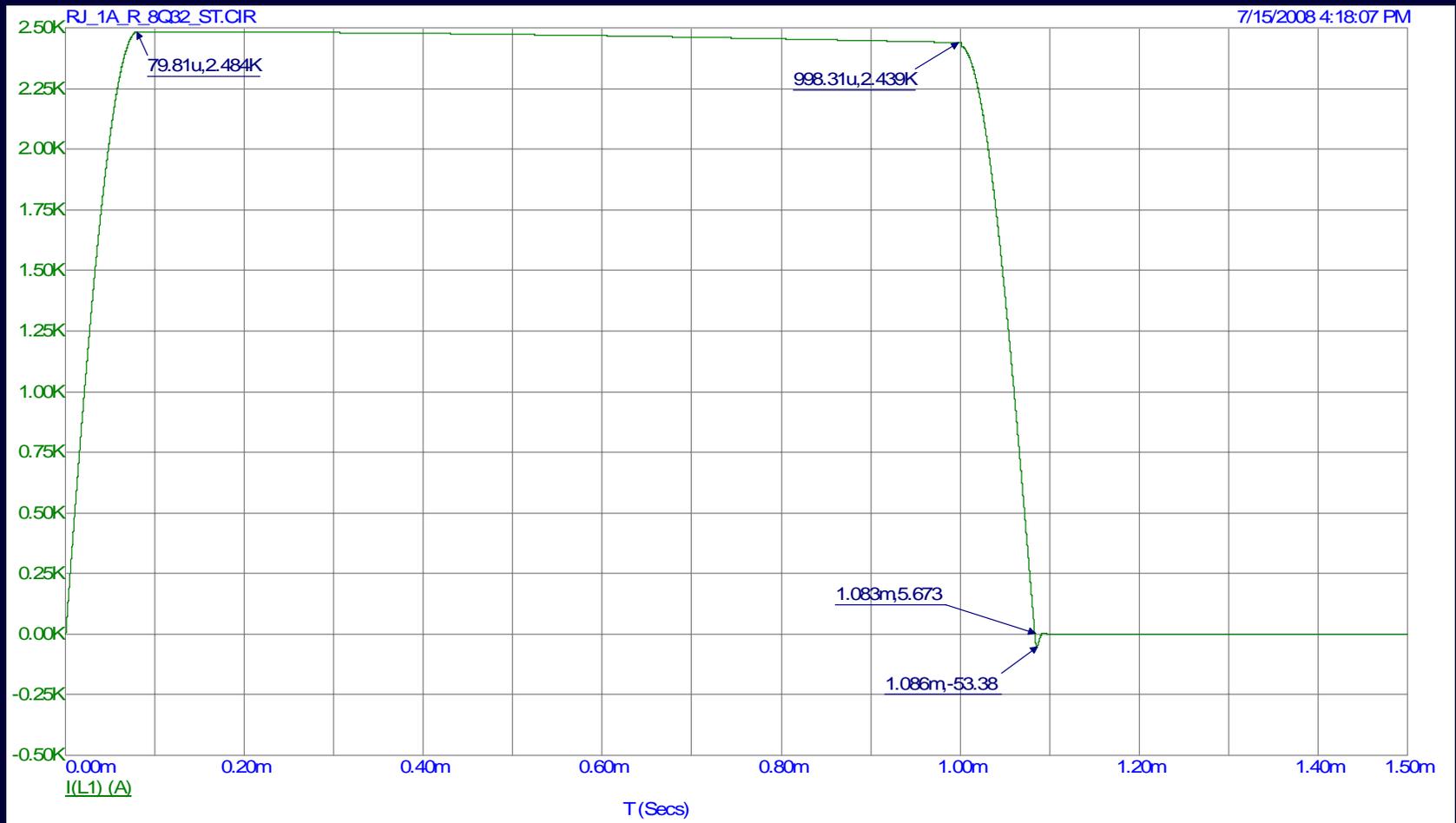

Simulation

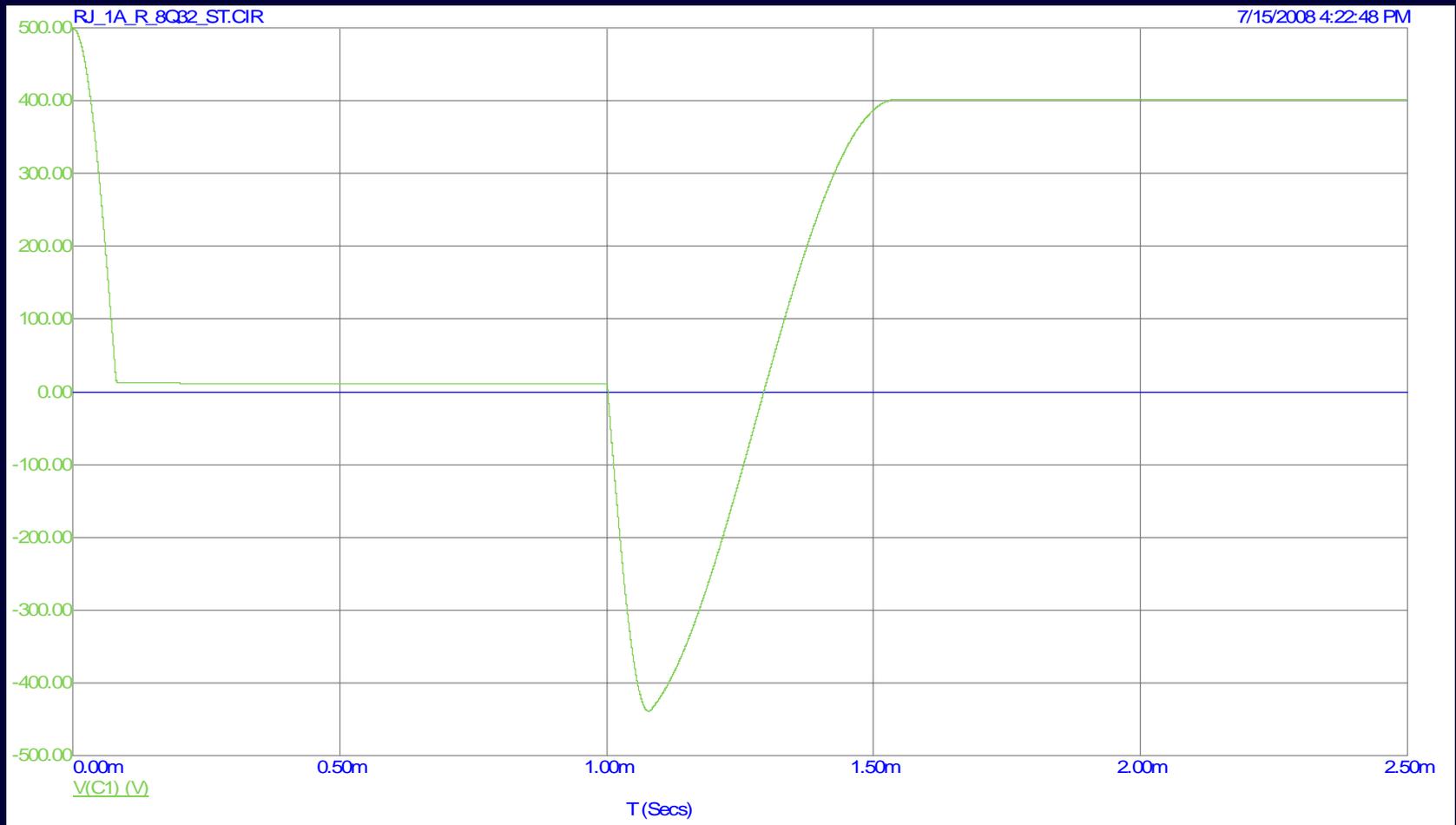


Resistance Effect

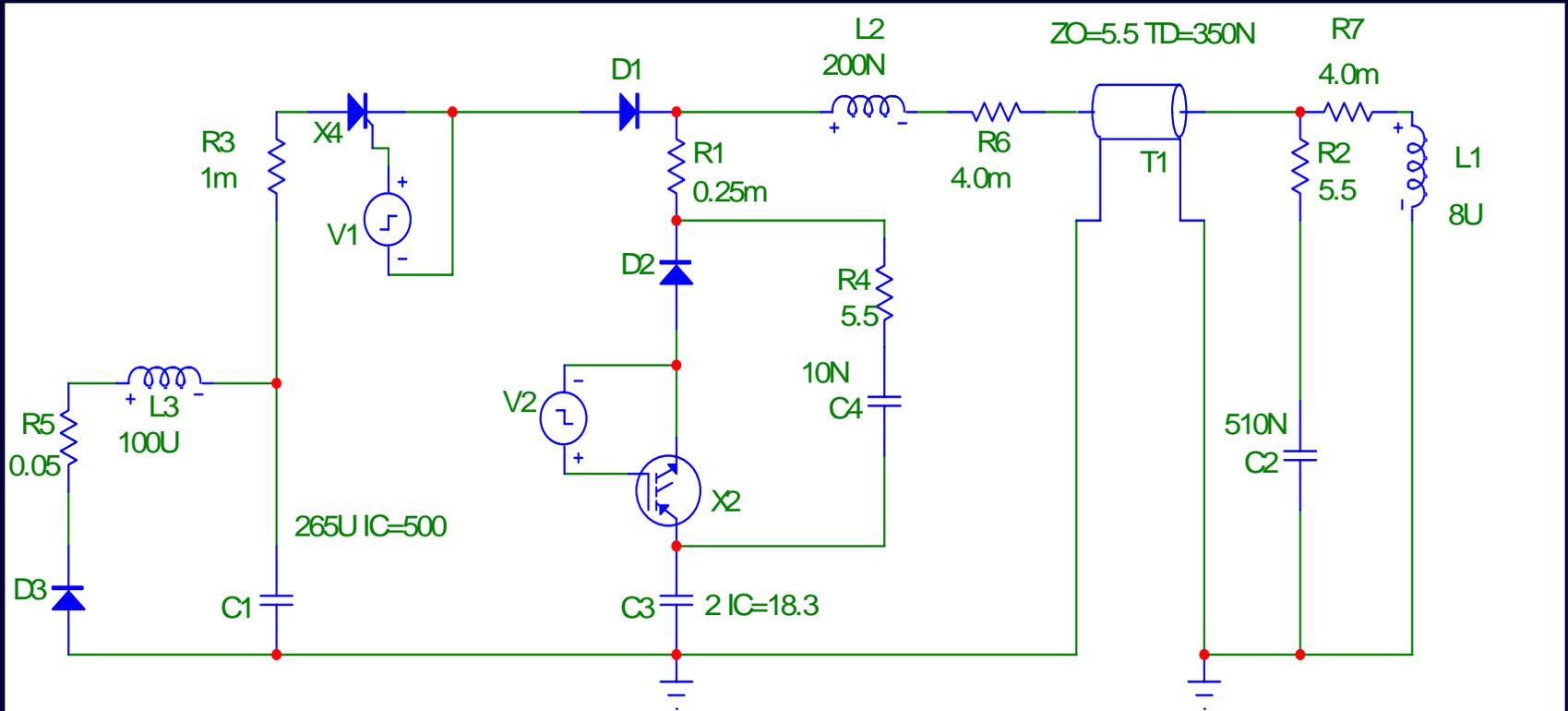


RJ_1A_R_8Q32_ST_R


Simulation

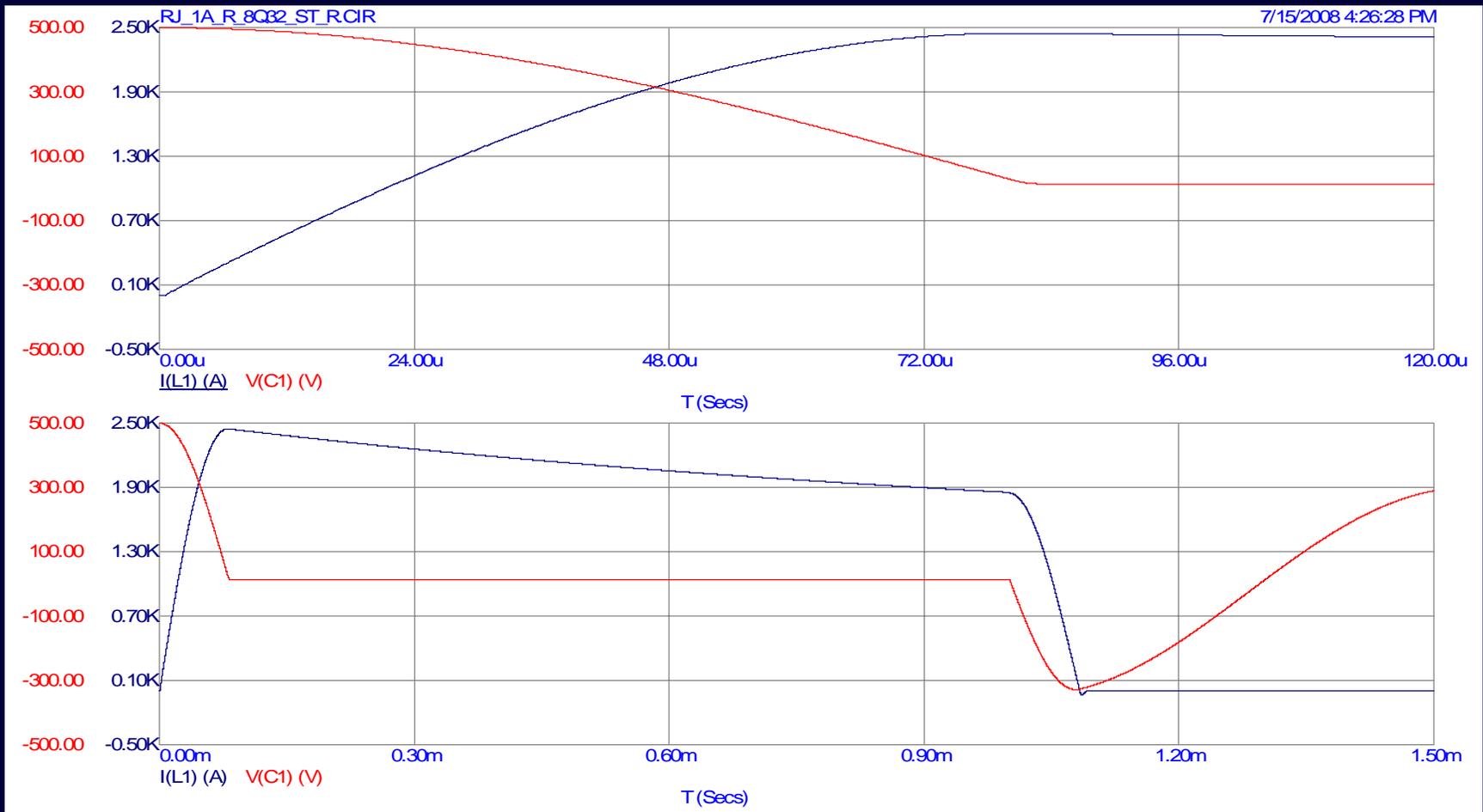


Simulation

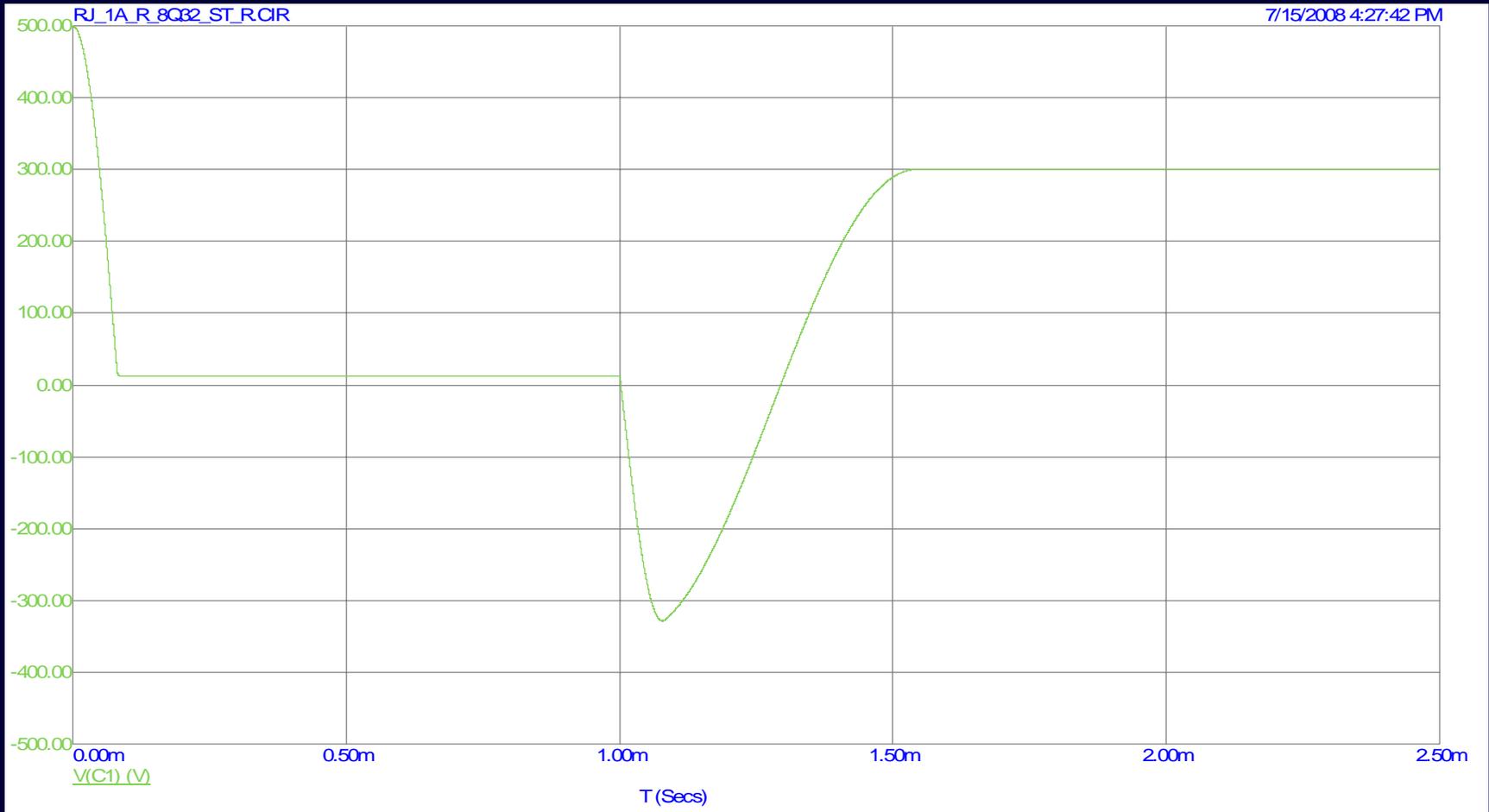

Load Inductance and Pulse Undershoot

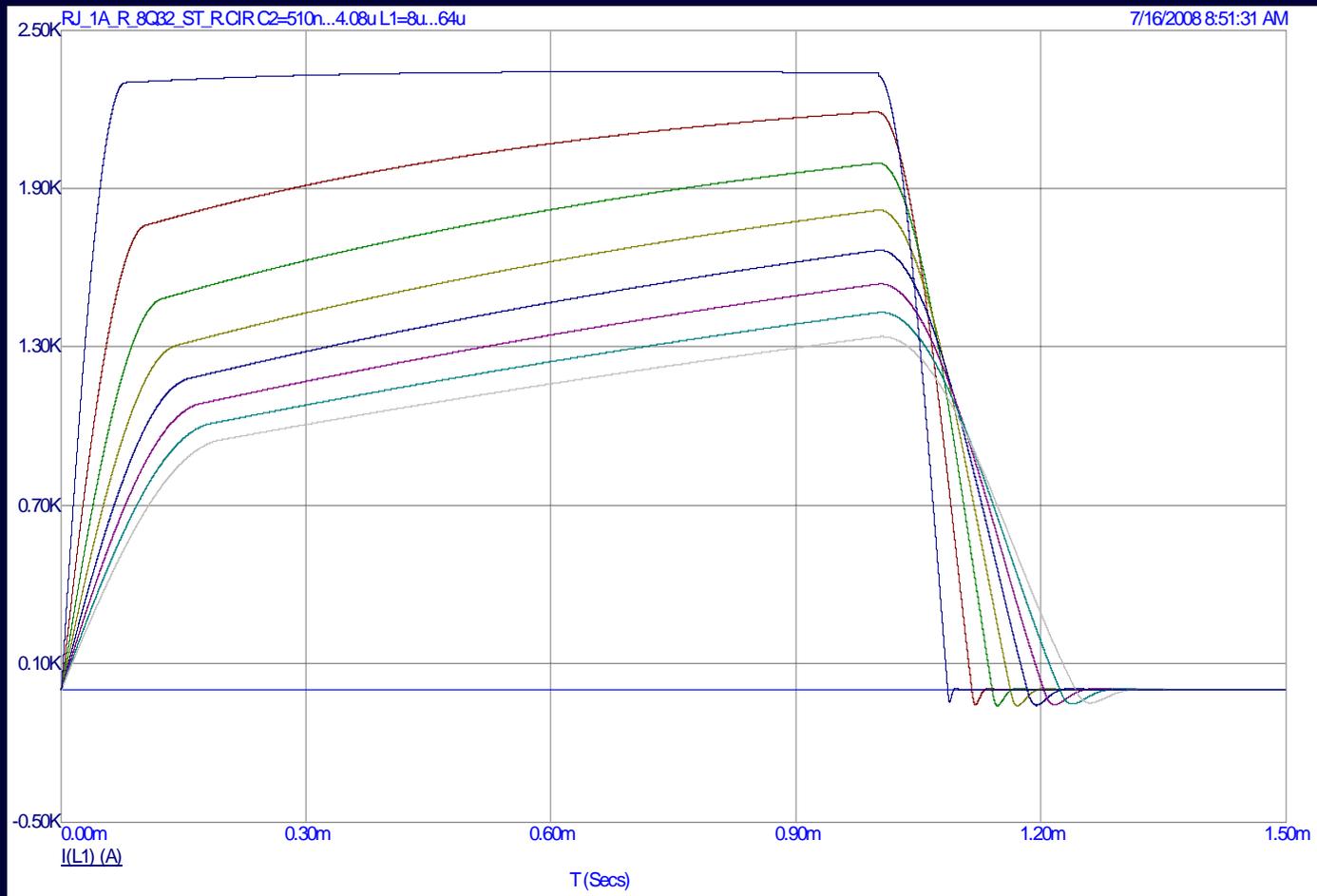


Proposed Schematic

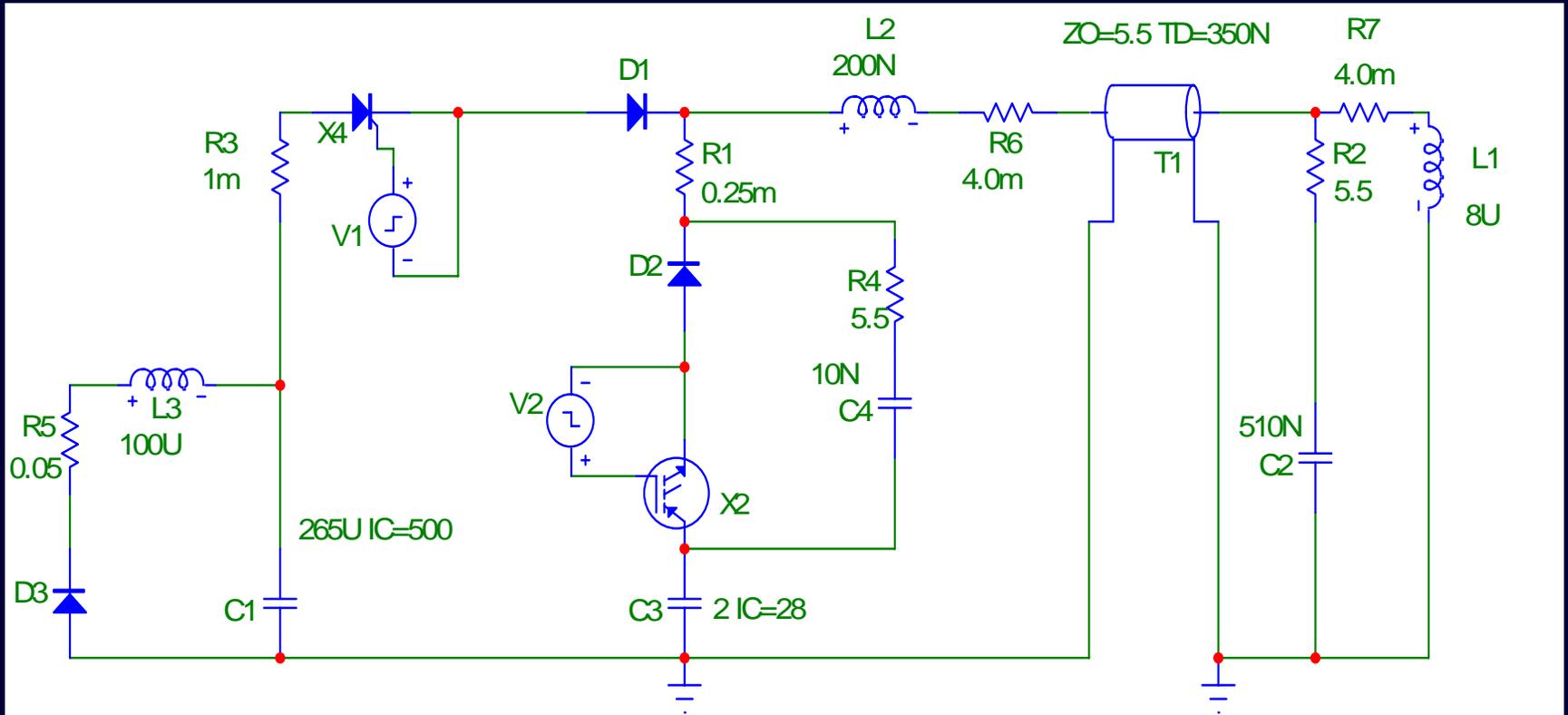


RJ_1A_R_8Q32_ST_R


Simulation

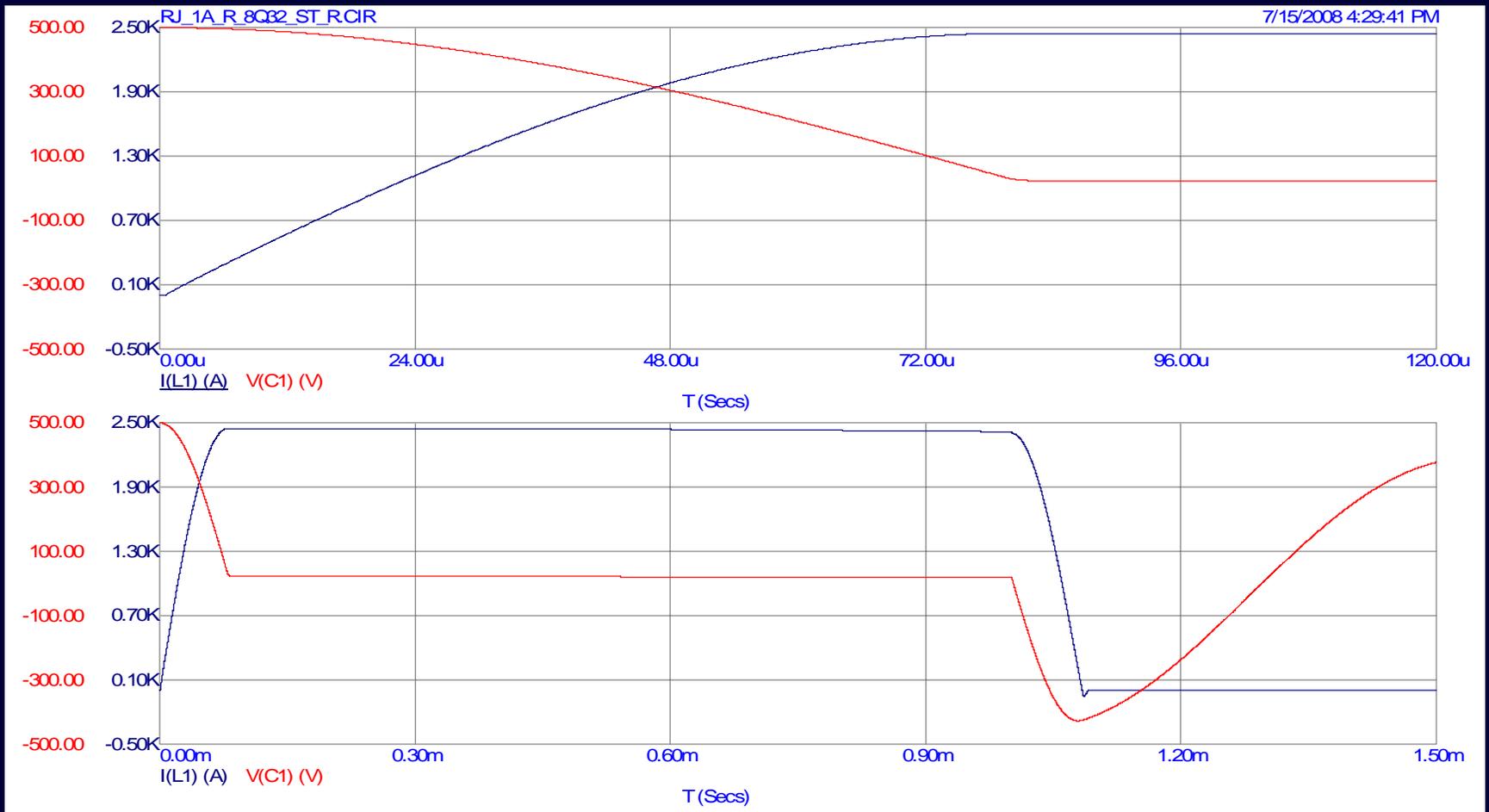


Simulation

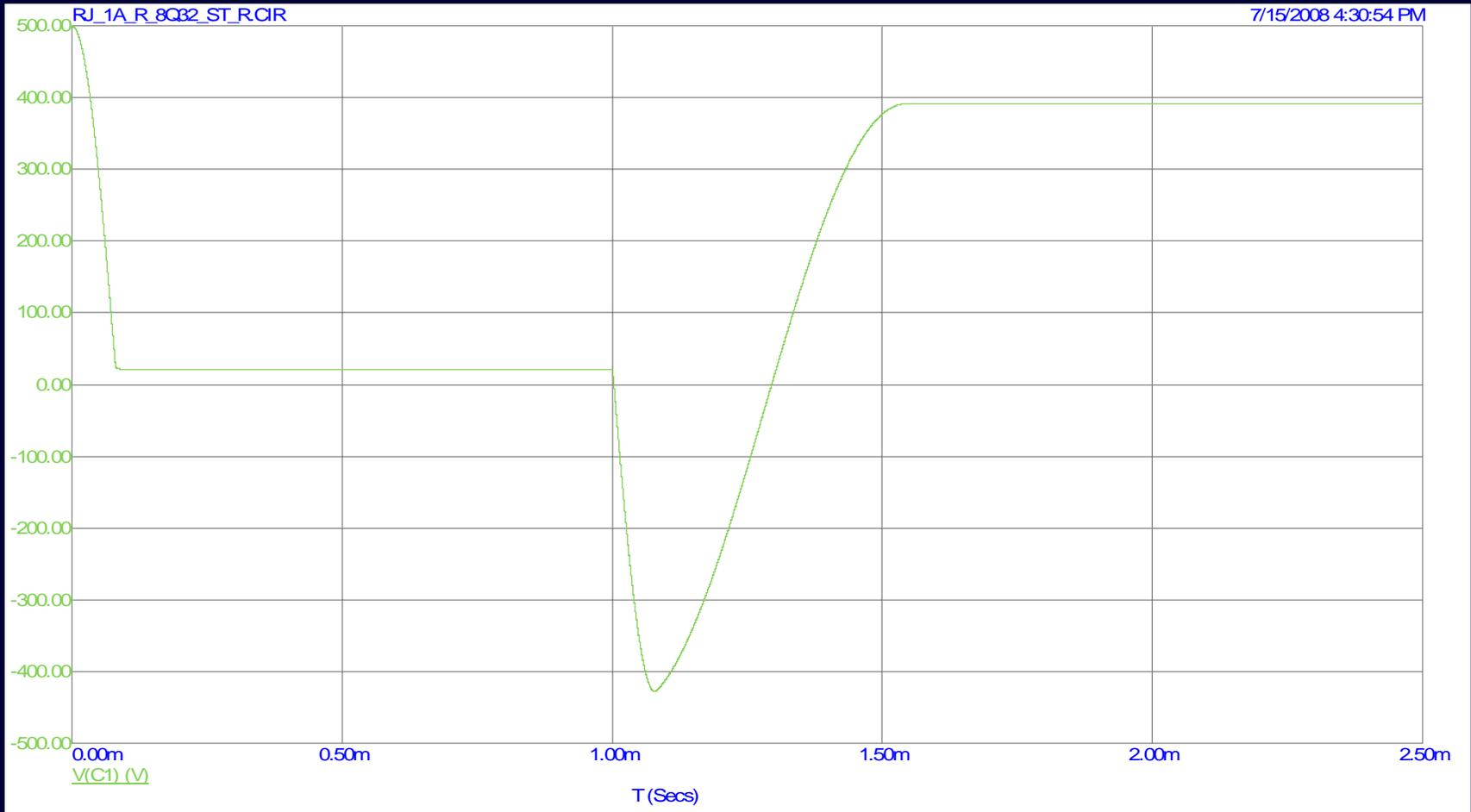


Larger Resistance

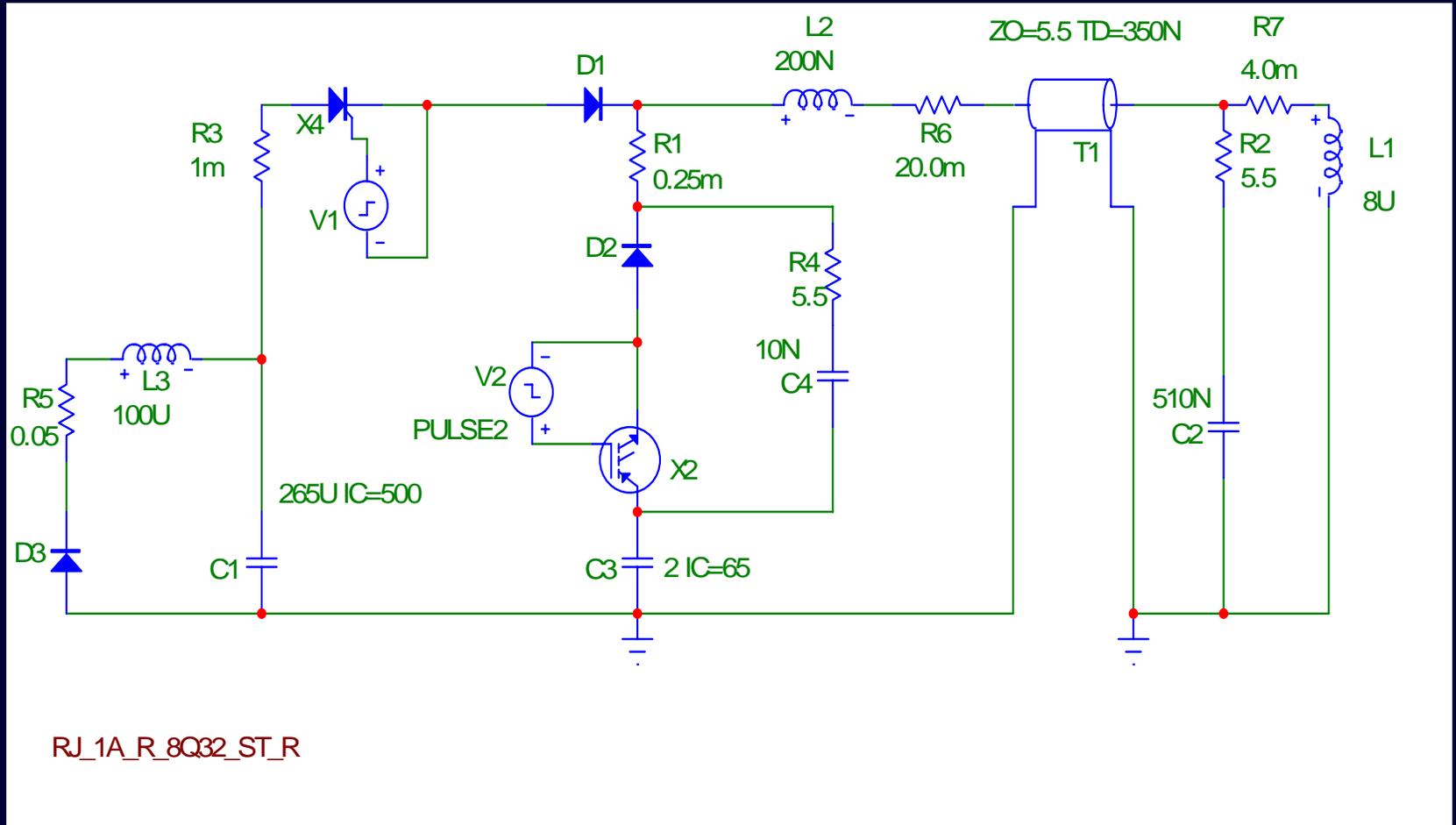


Larger Resistance

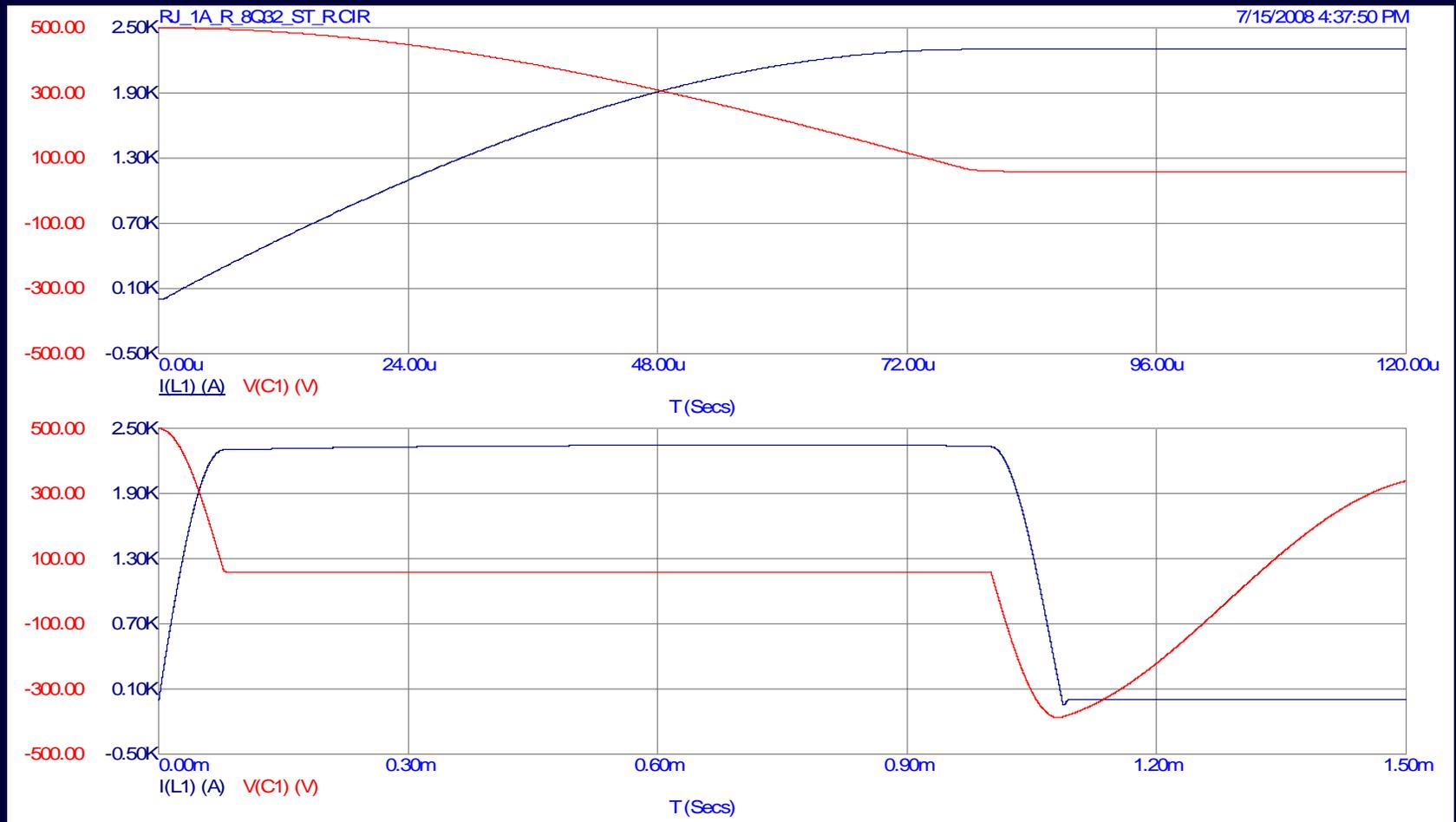


Larger Resistance

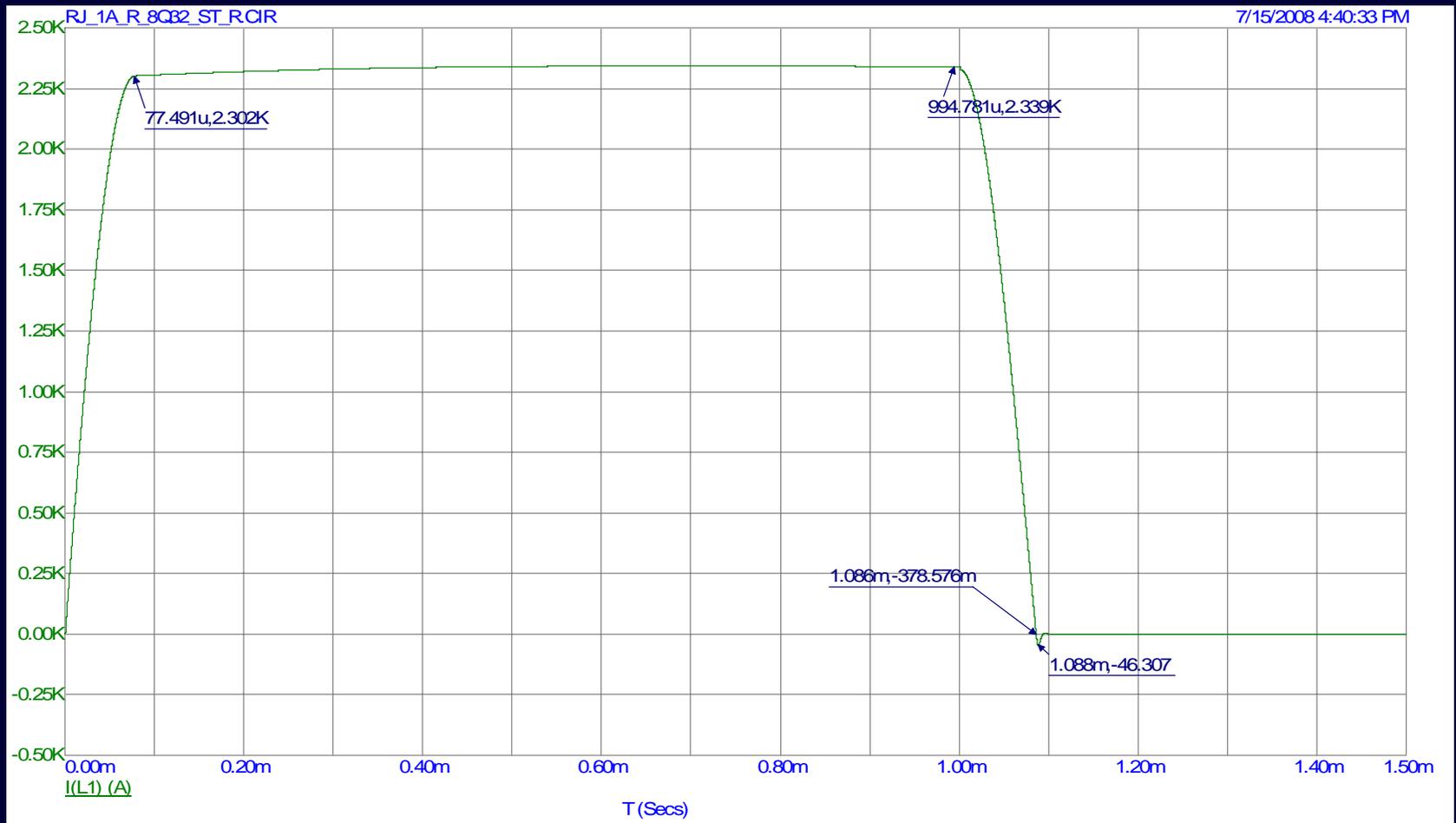


Larger Resistance

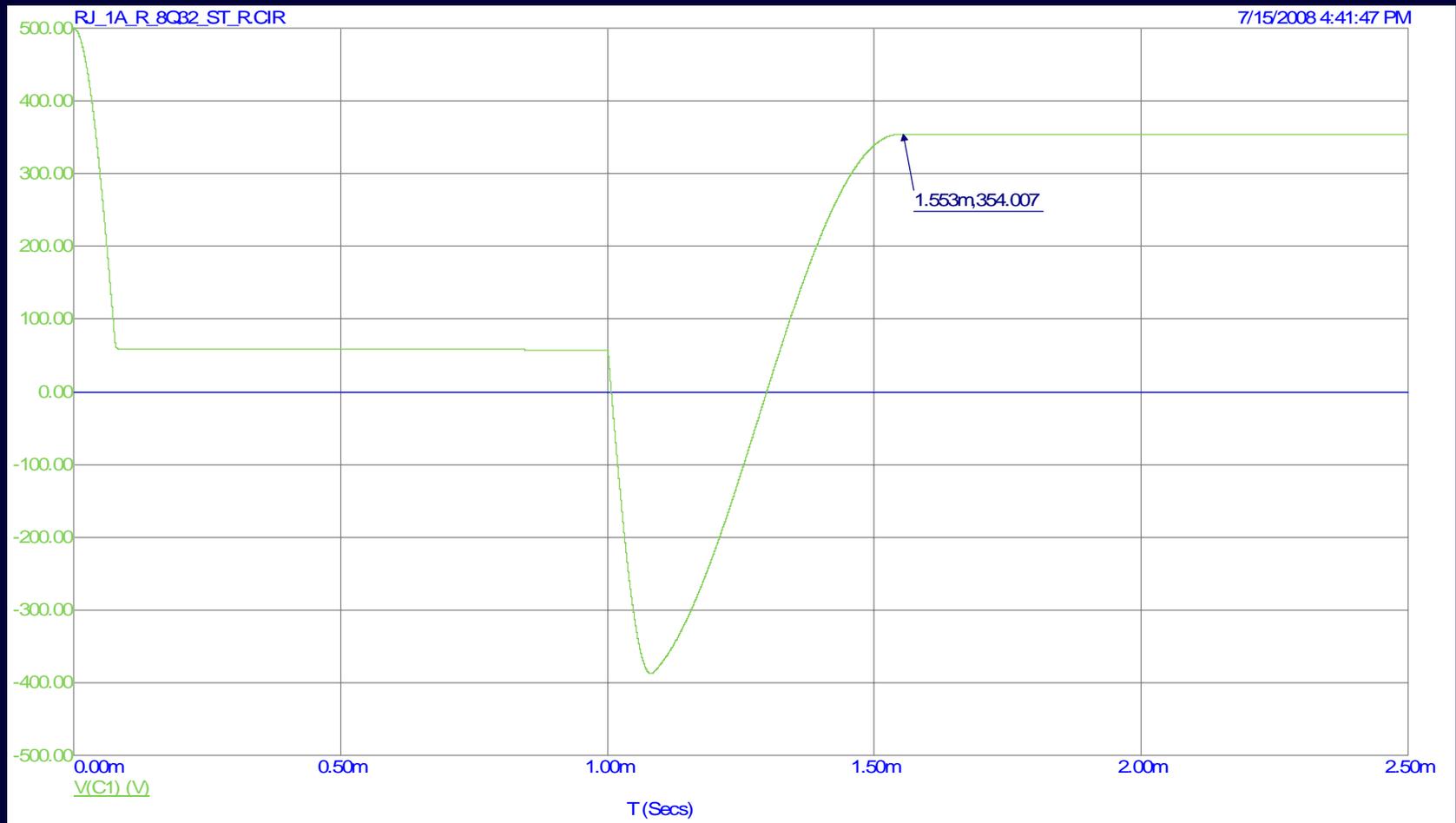


Long Pulse

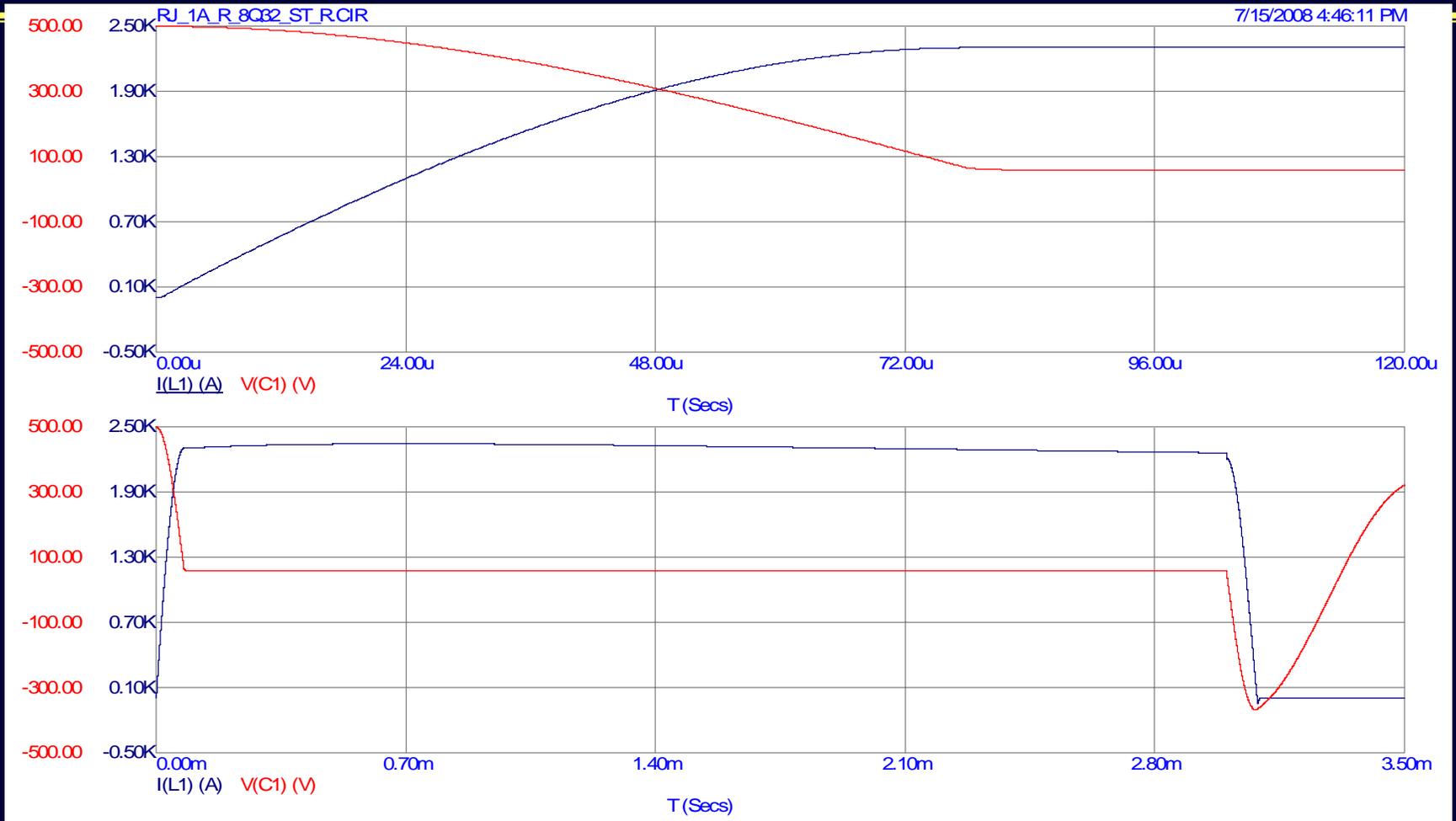


Long Pulse

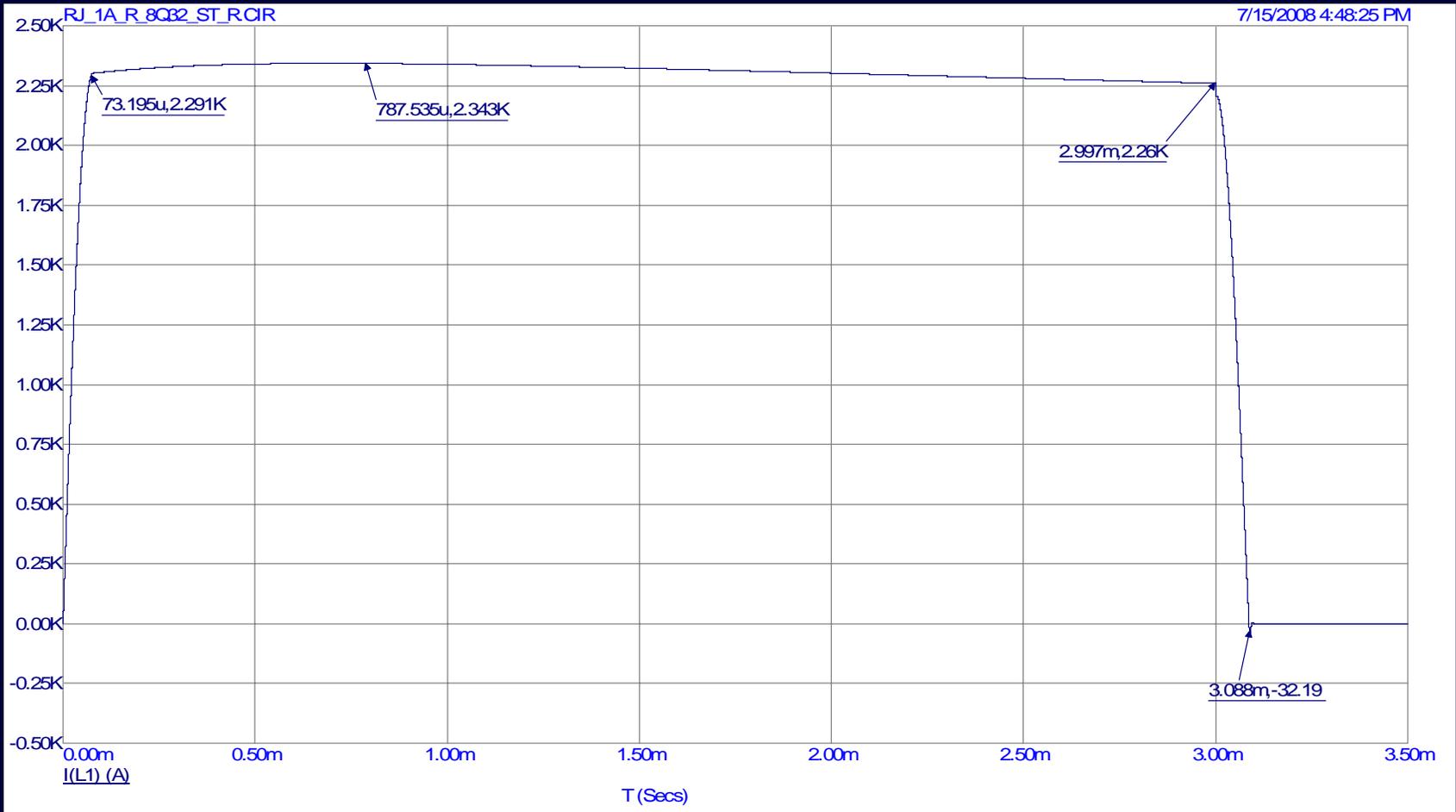

Long Pulse

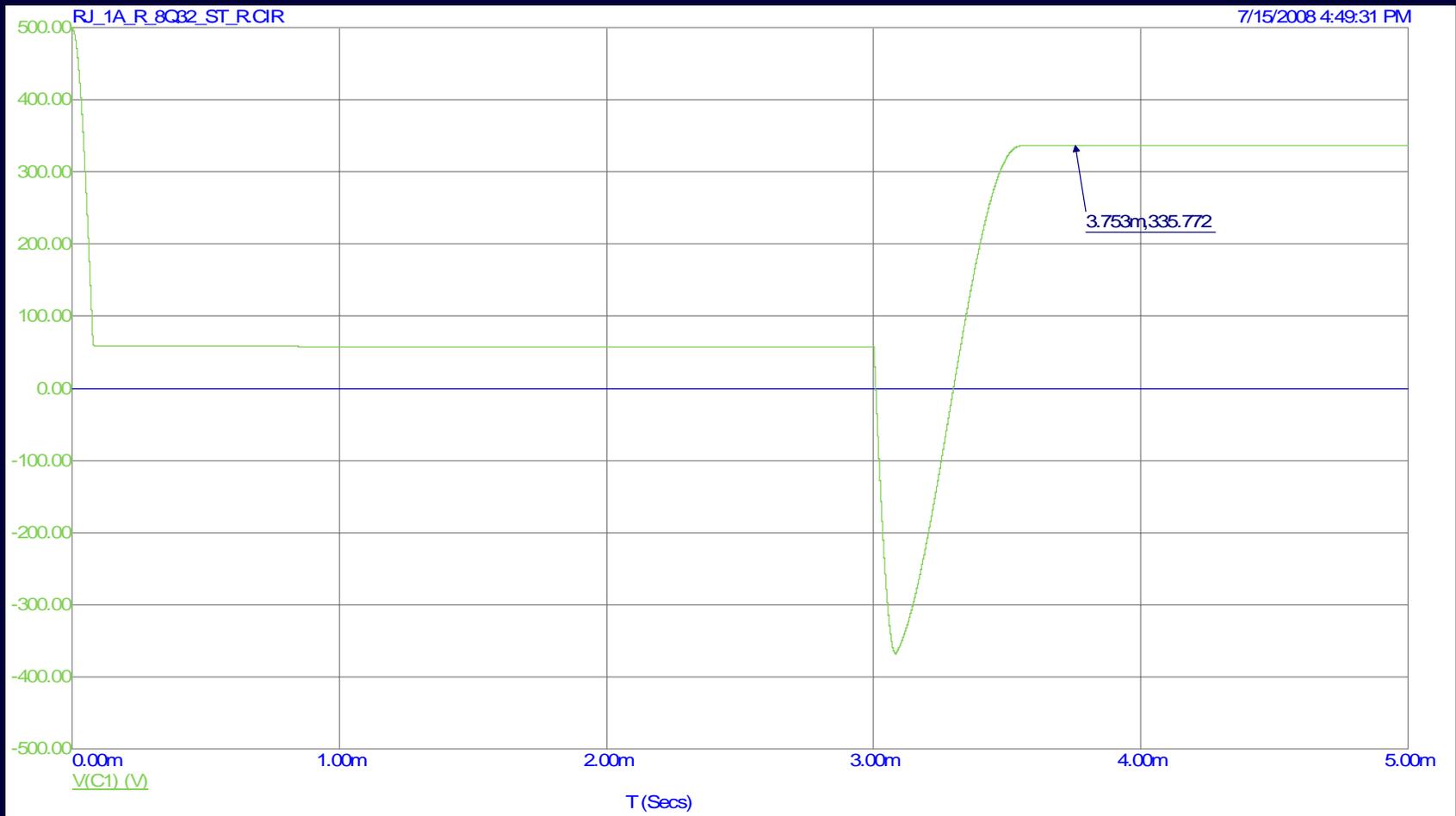


Parasitic Inductance Effect

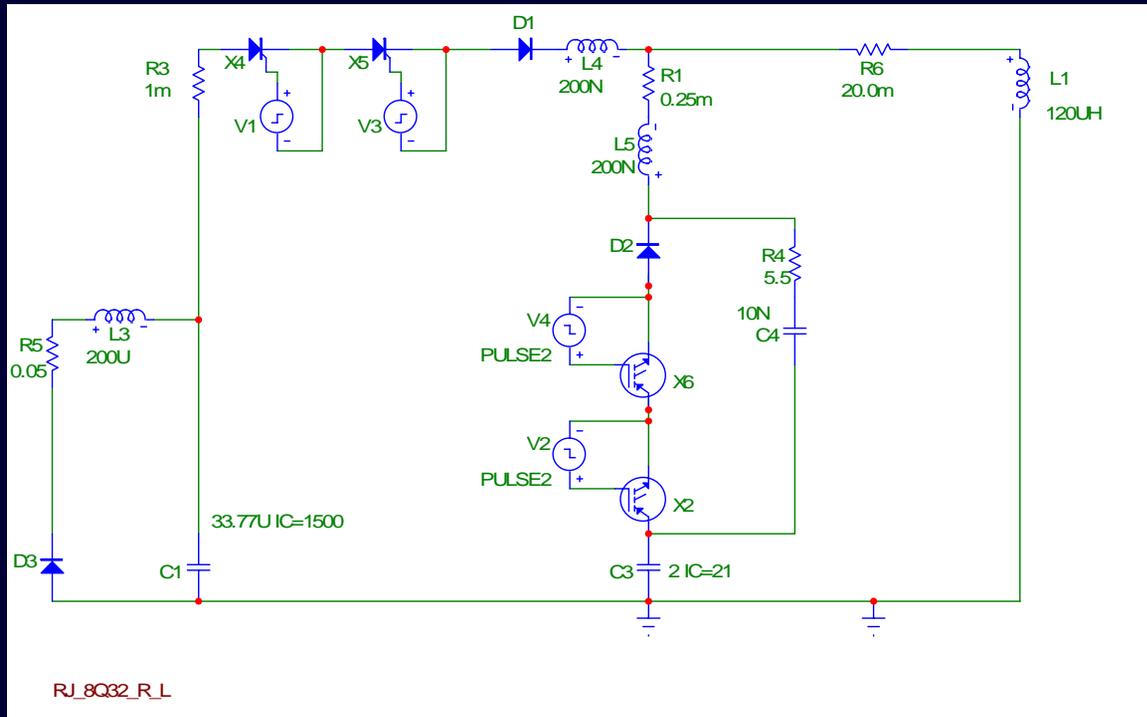


Parasitic Inductance Effect

Simulation

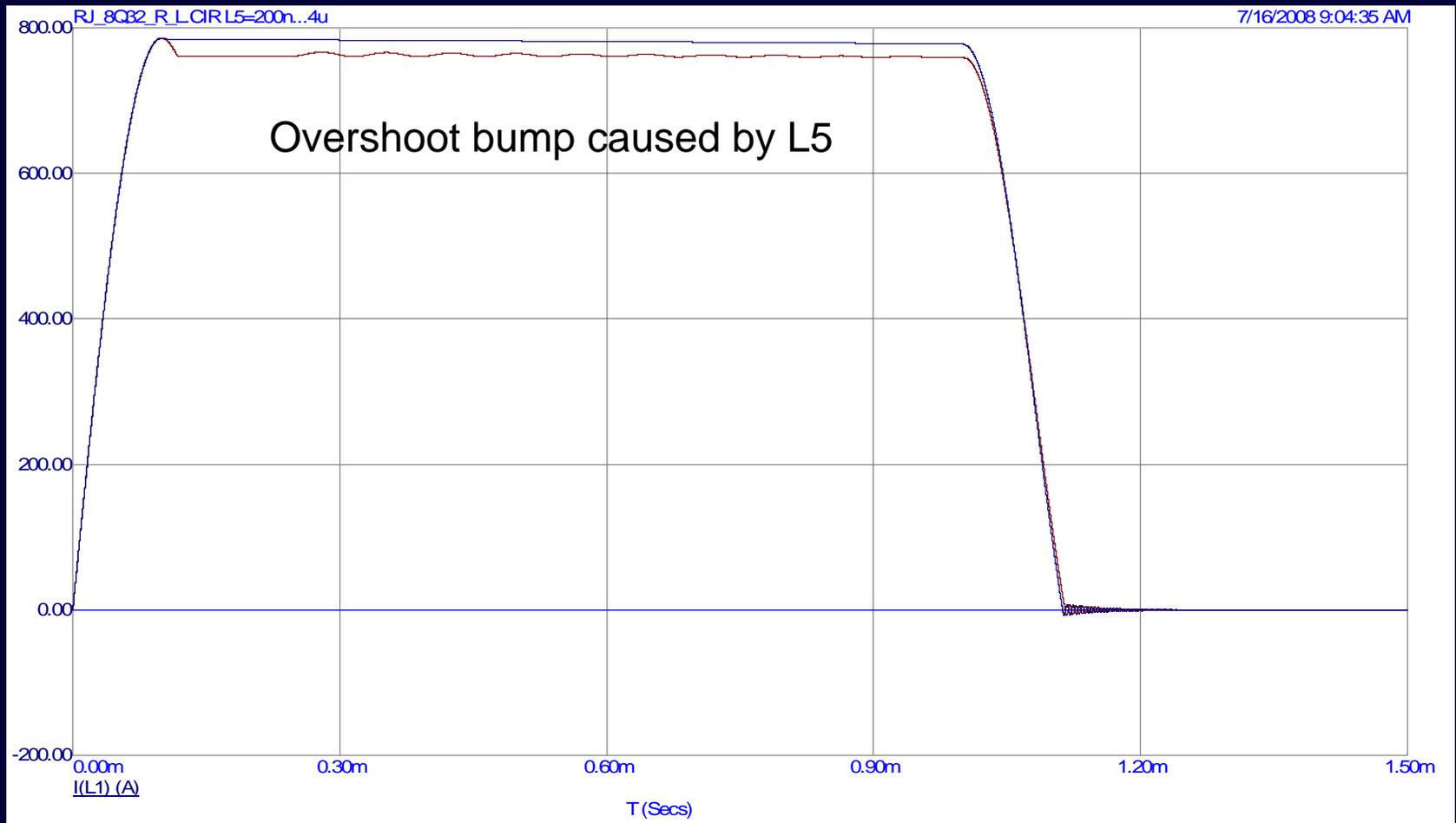

Simulation

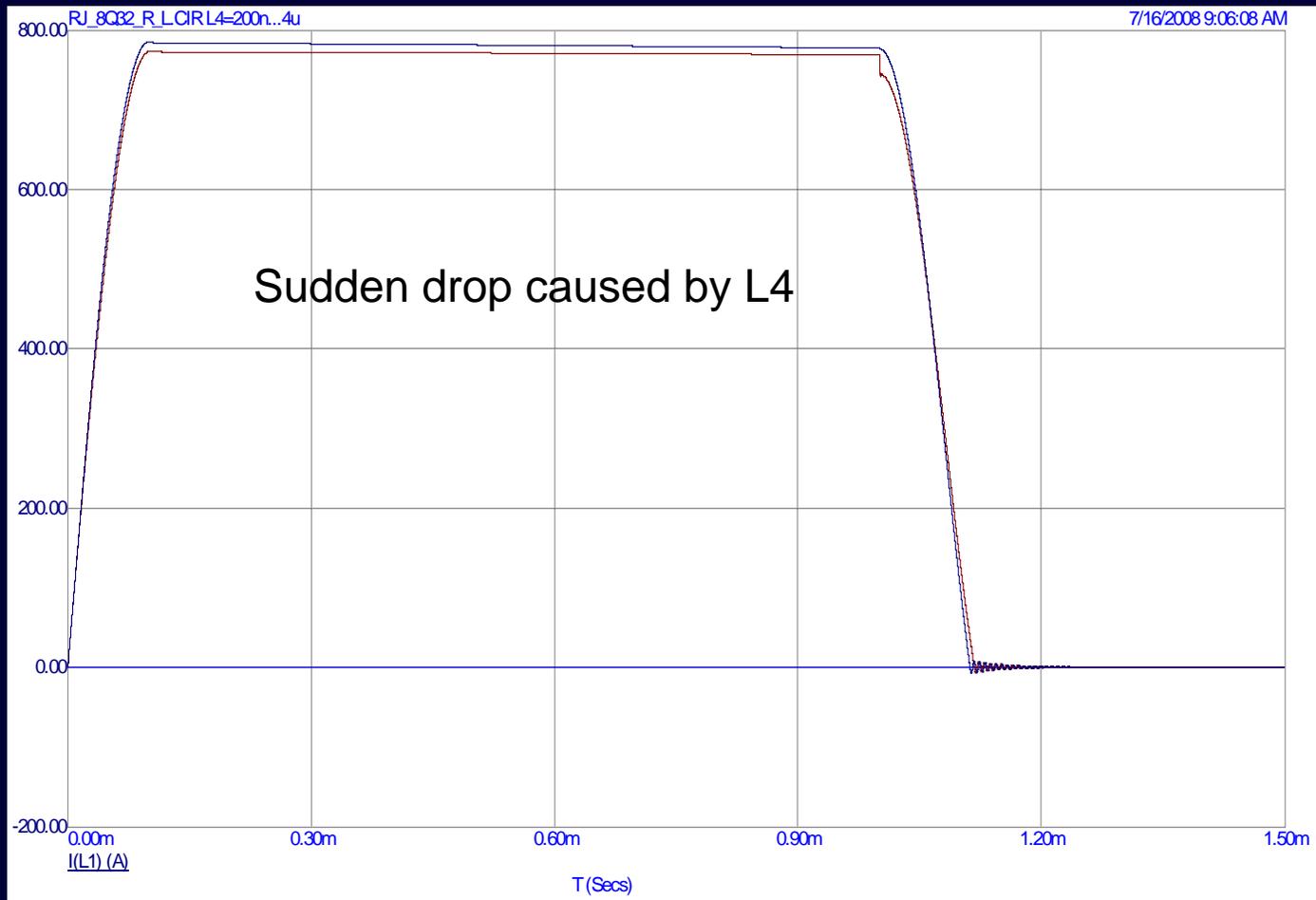

Cable Inductance

- Cable inductance can be reduced by using Coaxial Cables
- Suggested cables
 - RG213
 - DSI 2241
 - DSI 2139
 - DSI 2255
- Coaxial cables have lower cost

Pulse Flat-top Flatness

- 10% seems to be reasonable to achieve

Pulse Rise/Fall Edge Symmetry

- Slight difference has been observed
- Fall time is ~10% longer than rise time
- Further investigation will be conducted

Pulse Overshoot

- Caused by parasitic inductance
- Lower loop inductance can reduce pulse overshoot
- → Construction and Layout with low inductance

Pulse Undershoot

- Might be caused by load inductance
- Higher the load inductance, bigger the pulse undershoot?
- Lower inductance preferred
- Further investigation

Resistance Effect

- Slight impact on peak current amplitude
- Larger impact on low voltage capacitor charging voltage
- Resistive heating
- Construction and layout with low resistive material and structure
- Components with low “ON” resistance

Conclusion

- Coaxial cable will lower total inductance
- Coaxial cable will lower main bank voltage
- Single turn coil will lower load inductance
 - With coaxial cable connection the main bank voltage will be lowered to within voltage rating of existing fast bump capacitor
 - Smaller undershoot
- Cooling method has to be investigated

Pulse Waveform Specifications

Option 2 – Bipolar Triangles

