

# AC-dipole Basic Design


Peter Oddo

December 20, 2007

# Assumptions


- 92.36 $\mu$ H inductance from 3D model
  - 100Gm @ 120A
- Estimated power dissipation, Q, and R<sub>S</sub> based on existing magnet
  - 319W, Q=510, 44.4mO @ 39kHz
  - 534W, Q=478, 74.1mO @ 61kHz
- Tuning is a function of reactive power
  - VA<sub>TUNING</sub>=VA<sub>LC</sub>\*(1-(F<sub>LO</sub>/F<sub>HI</sub>)<sup>2</sup>)

# Basic Circuit

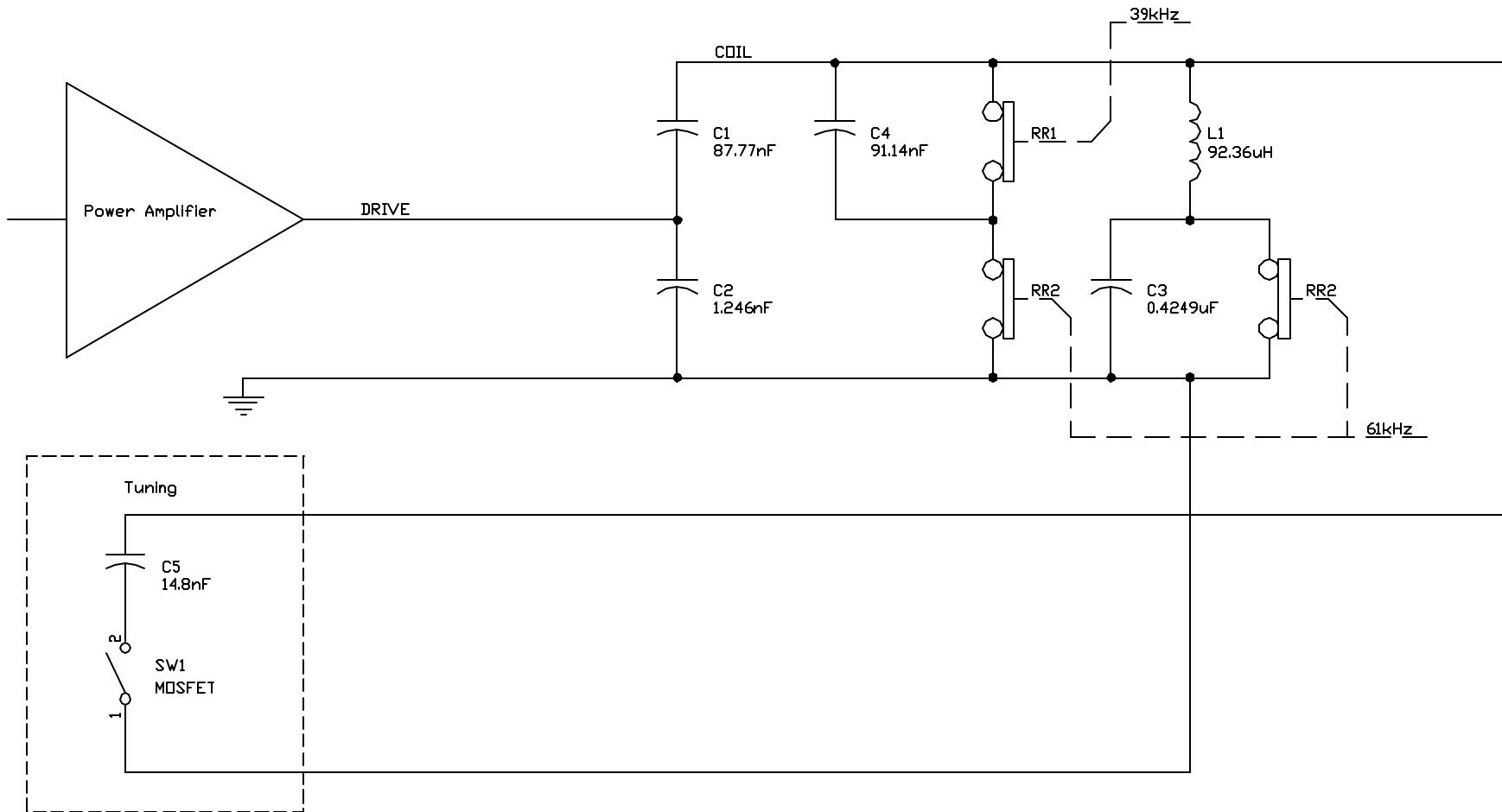
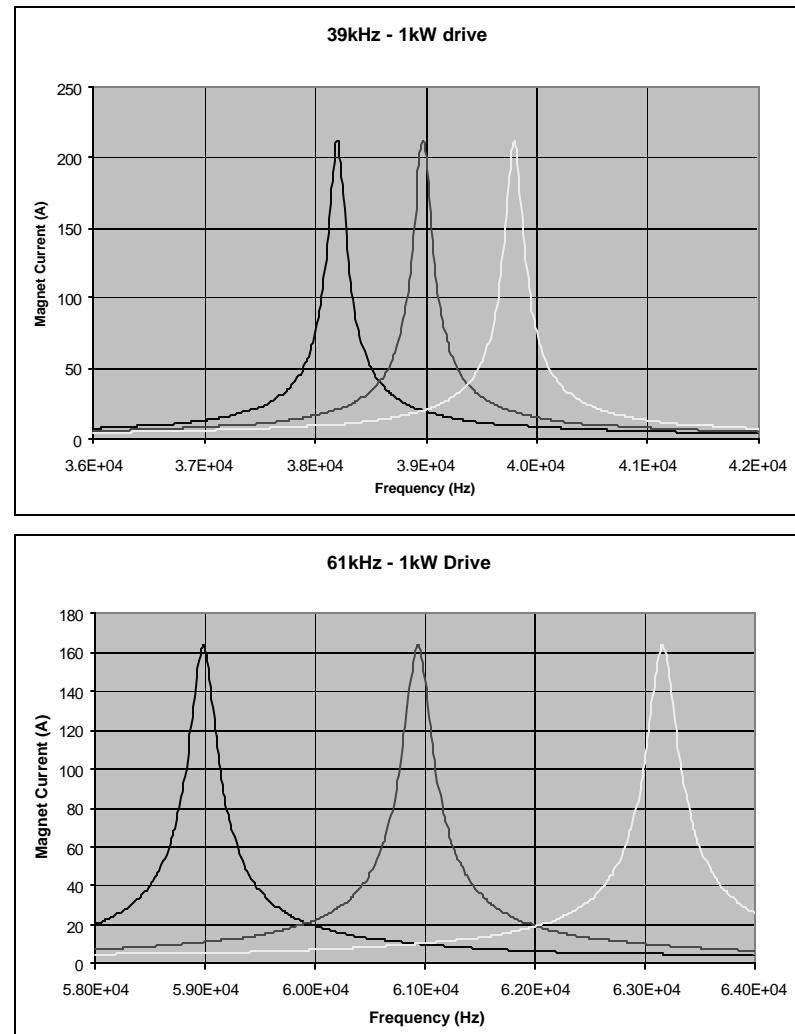
# Simulated Performance

- Sufficient current headroom at 1kW
  - 212A @ 39kHz
  - 161A @ 61kHz
- ? F wider at 61kHz
  - ? F  $\pm$ 800Hz @ 39kHz
  - ? F  $\pm$ 2090Hz @ 61kHz
- $50\Omega \pm 5\Omega$  impedance over range
- $V_{PK} < 5kV_{PK}$



# Next Step

- Test tuning at 1kW
  - Complete test setup
  - Complete FPGA code & software driver